

Course Name: Digital Hardware Design
Course Code: 17B1NEC741

Finite State Machine-2


Dr. Arti Noor
Dean, Academic Affairs
Electronics and Communication Engineering,
Jaypee Institute of Information Technology, Noida

Example 3

- Use the characteristic table or characteristic equation of the JK FF, i.e., $Q(t+1) = JQ' + K'Q$ to find the next state.
- Derive the state transition table.
- In this case there is no output.

$$J_A = B, K_A = X'B$$

$$J_B = X', K_B = X \oplus A$$

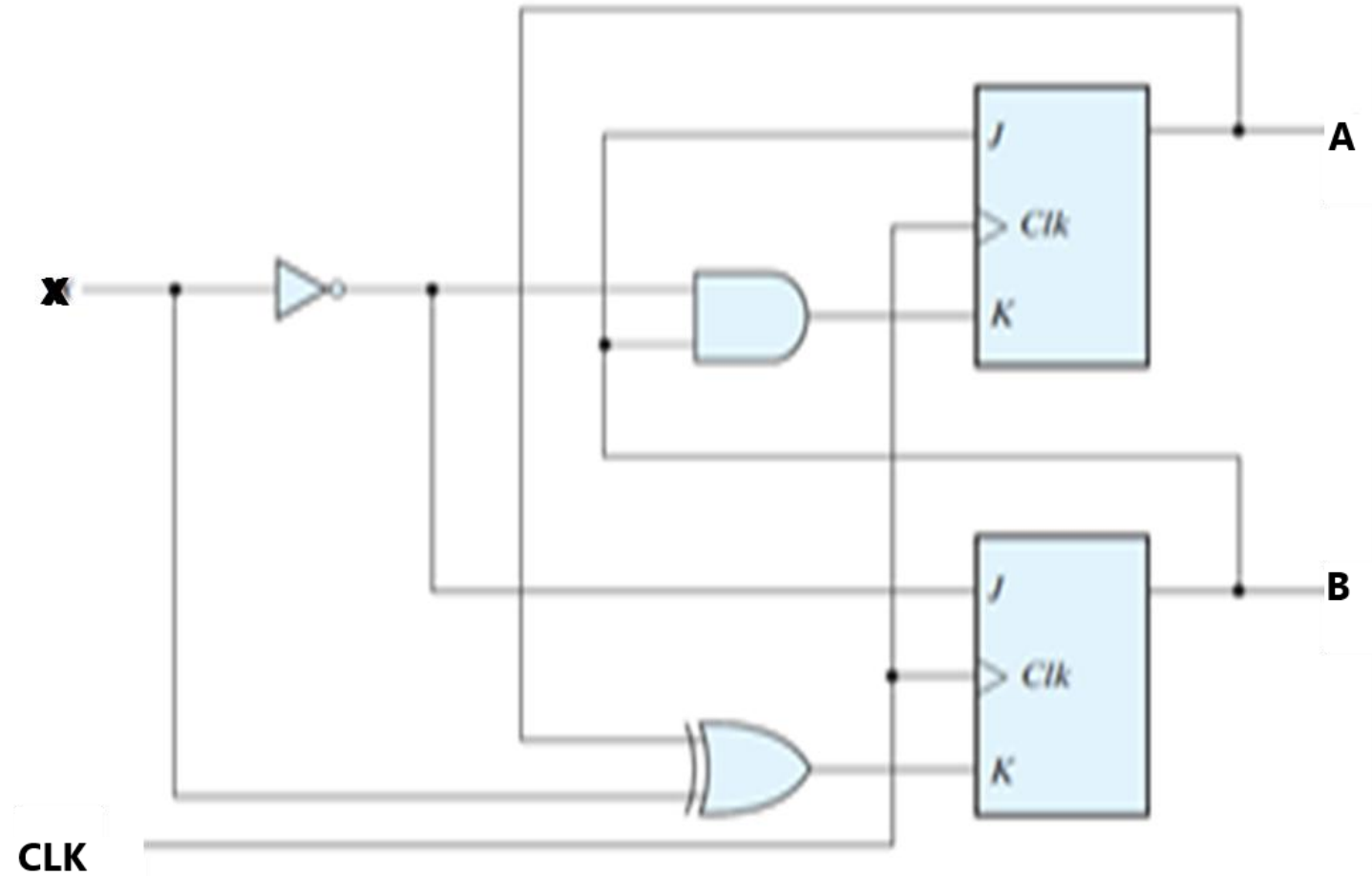

Example 3

Not part of state table

Current state		Input	FF Inputs				Next state	
$A(t)$	$B(t)$	$x(t)$	J_A	K_A	J_B	K_B	$A(t+1)$	$B(t+1)$
0	0	0	0	0	1	0	0	1
0	0	1	0	0	0	1	0	0
0	1	0	1	1	1	0	1	1
0	1	1	1	0	0	1	1	0
1	0	0	0	0	1	1	1	1
1	0	1	0	0	0	0	1	0
1	1	0	1	1	1	1	0	0
1	1	1	1	0	0	0	1	1


Present State	Next State	Inputs	
Q	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

$$A(t+1) = J_A A' + K'_A A$$

$$B(t+1) = J_B B' + K'_B B$$

Example 3


Present State		Input x	Next State	
A	B		A	B
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

 


State diagram

Difference between Mealy and Moore

 Example: State Machine '10' Sequence Detector



Moore Machine

 

Mealy Machine

State Machine Sequence Detector

Sequence detector is of two types:

1. Overlapping
2. Non-Overlapping

Overlapping: In this type, the last bit of one sequence becomes the first bit of the next.

Non-Overlapping: In this type, the last bit of one sequence does not become the first bit of the next sequence.

Example: 101 Mealy sequence detector

For non-overlapping case

Input :0110101011001

Output:0000**1**000**1**0000

For overlapping case

Input :0110101011001

Output:0000**1**0**1**0**1**0000

FSM Design (Moore)

Problem Statement:

Design a FSM that detects a sequence of three or more consecutive ones on an input bit stream.

The FSM should output a 1 when the sequence is detected, and a 0 otherwise.

Input: 0 1 1 1 0 1 0 1 1 0 1 1 1 0 1 ...


Non-Overlapping Case

Output: 0 0 0 1 0 0 0 0 0 0 0 0 0 1 0 0


...

FSM Design (Moore)

 Input: 0 1 1 1 0 1 0 1 1 0 1 1 1 0 1 ...
 Output: 0 0 0 **1** 0 0 0 0 0 0 0 0 0 **1** 0 0
 ...



FSM Design (Moore)

 

Present State		Input x	Next State		Output y
Q_A	Q_B		Q_A^+	Q_B^+	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1


FSM Design (Moore)

Synthesis using D Flip Flop


Present State		Input	Next State		Flip-Flop Input	
Q_A	Q_B		Q_A^+	Q_B^+	D_A	D_B
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	0	0	0	0
0	1	1	1	0	1	0
1	0	0	0	0	0	0
1	0	1	1	1	1	1
1	1	0	0	0	0	0
1	1	1	1	1	1	1

FSM Design (Moore)


Synthesis using D Flip Flop

 

$$D_A = Ax + Bx$$

 

$$D_B = Ax + B'x$$

 

$$y = AB$$


FSM Design (Moore)

Synthesis using D Flip Flop

$$D_A = Ax + Bx \quad D_B = Ax + B'x$$

$$y = AB$$

$$A = Q_A, \quad B = Q_B$$

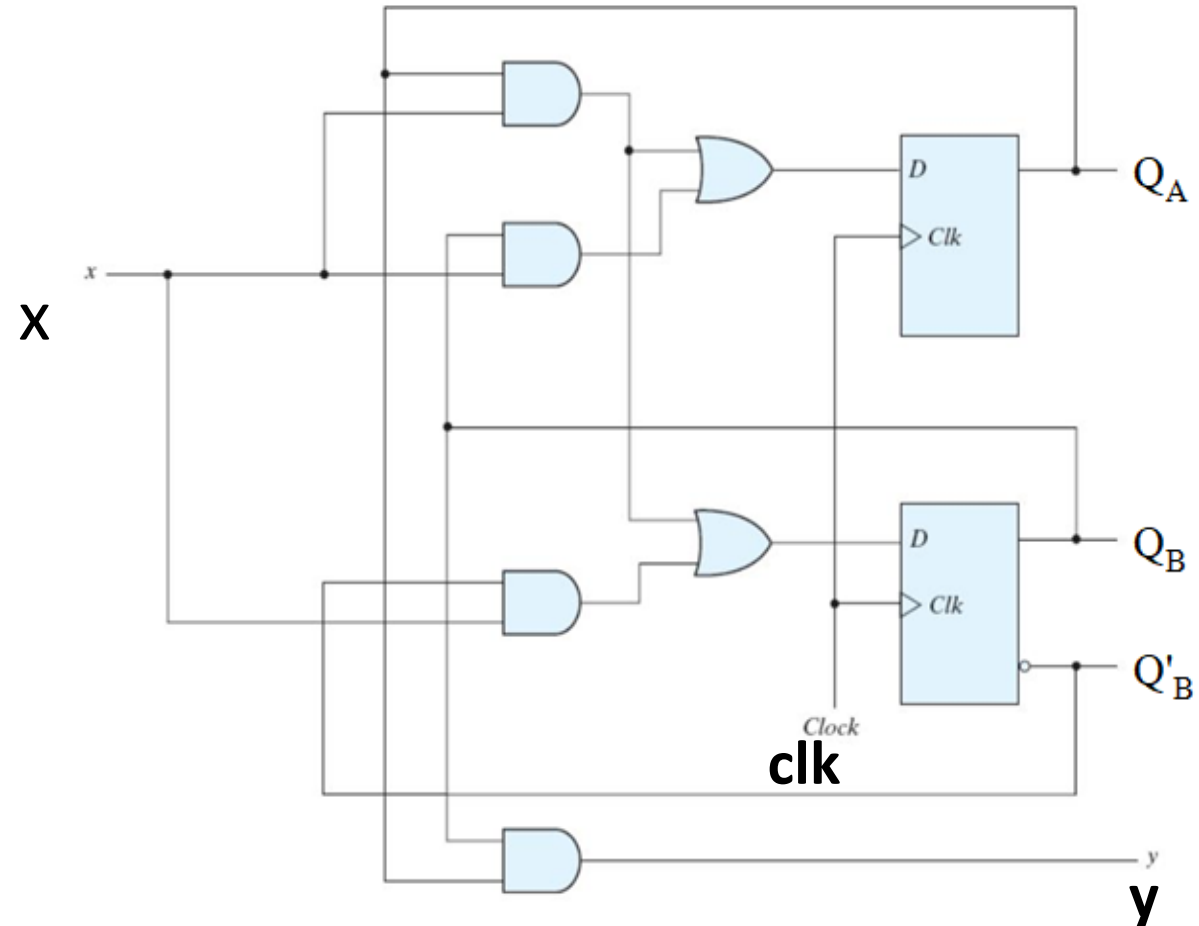

FSM Design (Moore)

Synthesis using JK Flip Flop

Present State	Next State	Inputs	
Q	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Present State		Input	Next State		Flip-Flop Inputs			
Q_A	Q_B	x	Q_A^+	Q_B^+	J_A	K_A	J_B	K_B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

FSM Design (Moore)

Synthesis using JK Flip Flop

A \ Bx		B			
		00	01	11	10
A	0	m_0	m_1	m_3	m_2 1
	1	m_4 X	m_5 X	m_7 X	m_6 X

$J_A = Bx'$

A \ Bx		B			
		00	01	11	10
A	0	m_0 X	m_1 X	m_3 X	m_2 X
	1	m_4	m_5	m_7 1	m_6

$K_A = Bx$

A \ Bx		B			
		00	01	11	10
A	0	m_0	m_1 1	m_3 X	m_2 X
	1	m_4	m_5 1	m_6 X	m_7 X

$J_B = x$

A \ Bx		B			
		00	01	11	10
A	0	m_0 X	m_1 X	m_3	m_2 1
	1	m_4 X	m_5 X	m_6 1	m_7

$K_B = (A \oplus x)'$

FSM Design (Moore)


Synthesis using JK Flip Flop

$$J_A = Bx'$$

$$K_A = Bx$$

$$J_B = x$$

$$K_B = (A \text{ XOR } x)'$$

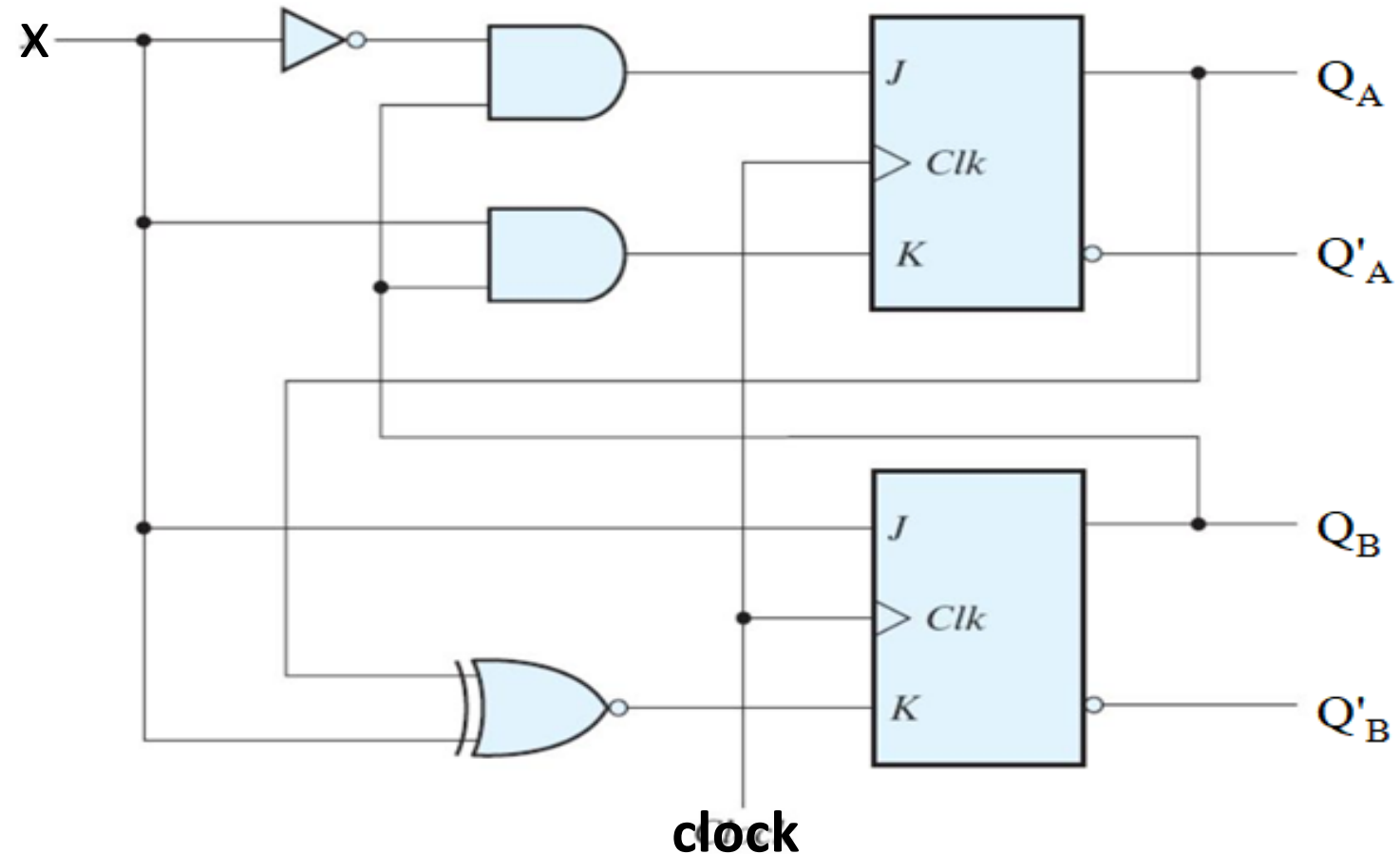

FSM Design Example 3 (Moore)

Design a Finite State Machine (FSM) that meets the following specifications:

1. The circuit has one input, w , and one output, z .
2. All changes in the circuit occur on the positive edge of the clock.
3. The output z is equal to 1 if the pattern 101 is detected on the input w . Otherwise, the value of z is equal to 0. Overlapping sequences **should** be detected.


Input (w): 0 0 0 1 0 1 0 1 1 0 1 1 0 1 1 ...

Output (z): 0 0 0 0 0 1 0 1 0 0 1 0 0 1 0 ...

FSM Design Example 3 (Moore)

Input (w): 0 0 0 1 0 1 0 1 1 0 1 1 0 1 1 ...

 Output (z): 0 0 0 0 0 1 0 1 0 0 1 0 0 1 0 ...



FSM Design Example 4 (Moore)

Design a Finite State Machine (FSM) that meets the following specifications:

1. The circuit has one input, w , and one output, z .
2. All changes in the circuit occur on the positive edge of the clock.
3. The output z is equal to 1 if the pattern 110 or the pattern 010 is detected on the input w . Otherwise, the value of z is equal to 0. Overlapping sequences **should** be detected.


Input (w): 0 1 0 0 1 1 0 1 0 1 1 1 0 1 1 ...

Output (z): 0 0 1 0 0 0 1 0 1 0 0 0 1 0 0 ...

FSM Design Example 4 (Moore)

Input (w): 0 1 0 0 1 1 0 1 0 1 1 1 0 1 1 ...

 Output (z): 0 0 1 0 0 0 1 0 1 0 0 0 1 0 0 ...



State
Diagram