

Course Name: Digital Hardware Design
Course Code: 17B1NEC741











Finite State Machine-3

Dr. Arti Noor

Dean, Academic Affairs

**Electronics and Communication Engineering,
Jaypee Institute of Information Technology, Noida**

Sequential Storage Units

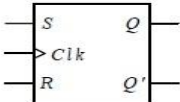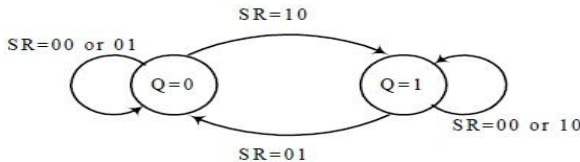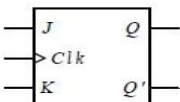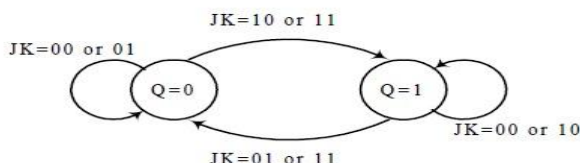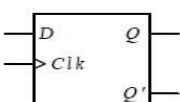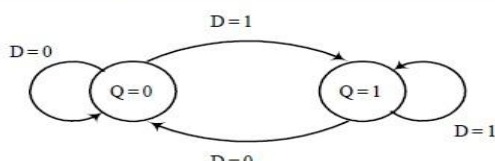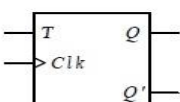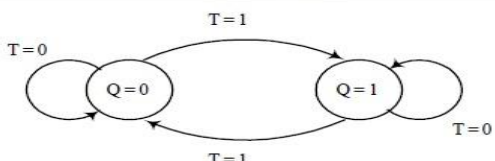Name / Symbol	Characteristic (Truth) Table	State Diagram / Characteristic Equations	Excitation Table																																																								
SR 	<table><tr><th>S</th><th>R</th><th>Q</th><th>Q_{next}</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>×</td></tr><tr><td>1</td><td>1</td><td>1</td><td>×</td></tr></table>	S	R	Q	Q _{next}	0	0	0	0	0	0	1	1	0	1	0	0	0	1	1	0	1	0	0	1	1	0	1	1	1	1	0	×	1	1	1	×	 $Q_{next} = S + R'Q$ $SR = 0$	<table><tr><th>Q</th><th>Q_{next}</th><th>S</th><th>R</th></tr><tr><td>0</td><td>0</td><td>0</td><td>×</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>×</td><td>0</td></tr></table>	Q	Q _{next}	S	R	0	0	0	×	0	1	1	0	1	0	0	1	1	1	×	0
S	R	Q	Q _{next}																																																								
0	0	0	0																																																								
0	0	1	1																																																								
0	1	0	0																																																								
0	1	1	0																																																								
1	0	0	1																																																								
1	0	1	1																																																								
1	1	0	×																																																								
1	1	1	×																																																								
Q	Q _{next}	S	R																																																								
0	0	0	×																																																								
0	1	1	0																																																								
1	0	0	1																																																								
1	1	×	0																																																								
JK 	<table><tr><th>J</th><th>K</th><th>Q</th><th>Q_{next}</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table>	J	K	Q	Q _{next}	0	0	0	0	0	0	1	1	0	1	0	0	0	1	1	0	1	0	0	1	1	0	1	1	1	1	0	1	1	1	1	0	 $Q_{next} = J'K'Q + JK' + JKQ'$ $= J'K'Q + JK'Q + JK'Q' + JKQ'$ $= K'Q(J' + J) + JQ'(K' + K)$ $= K'Q + JQ'$	<table><tr><th>Q</th><th>Q_{next}</th><th>J</th><th>K</th></tr><tr><td>0</td><td>0</td><td>0</td><td>×</td></tr><tr><td>0</td><td>1</td><td>1</td><td>×</td></tr><tr><td>1</td><td>0</td><td>×</td><td>1</td></tr><tr><td>1</td><td>1</td><td>×</td><td>0</td></tr></table>	Q	Q _{next}	J	K	0	0	0	×	0	1	1	×	1	0	×	1	1	1	×	0
J	K	Q	Q _{next}																																																								
0	0	0	0																																																								
0	0	1	1																																																								
0	1	0	0																																																								
0	1	1	0																																																								
1	0	0	1																																																								
1	0	1	1																																																								
1	1	0	1																																																								
1	1	1	0																																																								
Q	Q _{next}	J	K																																																								
0	0	0	×																																																								
0	1	1	×																																																								
1	0	×	1																																																								
1	1	×	0																																																								
D 	<table><tr><th>D</th><th>Q</th><th>Q_{next}</th></tr><tr><td>0</td><td>×</td><td>0</td></tr><tr><td>1</td><td>×</td><td>1</td></tr></table>	D	Q	Q _{next}	0	×	0	1	×	1	 $Q_{next} = D$	<table><tr><th>Q</th><th>Q_{next}</th><th>D</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	Q	Q _{next}	D	0	0	0	0	1	1	1	0	0	1	1	1																																
D	Q	Q _{next}																																																									
0	×	0																																																									
1	×	1																																																									
Q	Q _{next}	D																																																									
0	0	0																																																									
0	1	1																																																									
1	0	0																																																									
1	1	1																																																									
T 	<table><tr><th>T</th><th>Q</th><th>Q_{next}</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	T	Q	Q _{next}	0	0	0	0	1	1	1	0	1	1	1	0	 $Q_{next} = TQ' + T'Q = T \oplus Q$	<table><tr><th>Q</th><th>Q_{next}</th><th>T</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	Q	Q _{next}	T	0	0	0	0	1	1	1	0	1	1	1	0																										
T	Q	Q _{next}																																																									
0	0	0																																																									
0	1	1																																																									
1	0	1																																																									
1	1	0																																																									
Q	Q _{next}	T																																																									
0	0	0																																																									
0	1	1																																																									
1	0	1																																																									
1	1	0																																																									

FSM Design Procedure

1. Understand specifications
2. Derive state diagram
3. Create state table
4. Perform state minimization (if necessary)
5. Encode states (state assignment)
6. Create state-assigned table
7. Select type of Flip-Flop to use
8. Determine Flip-Flop input equations and FSM output equation(s)
9. Draw logic diagram

FSM Design Example 1 (Mealy)

1. Understand specifications

Design a FSM that detects a sequence of three or more consecutive ones on an input bit stream.


The FSM should output a 1 when the sequence is detected, and a 0 otherwise.

Input: 0 1 1 1 0 1 0 1 1 0 1 1 1 0 1 ...

Output: 0 0 0 1 0 0 0 0 0 0 0 0 0 1 0 0

FSM Design Example 1 (Mealy)

2. Derive state diagram

 

FSM Design Example 1 (Mealy)

3. Create state table
4. Perform state minimization (if necessary)
5. Encode states (state assignment)

Present State			Next State						Output	
			w = 0			w = 1			w = 0	w = 1
	Q_A	Q_B		Q_A^+	Q_B^+		Q_A^+	Q_B^+	z	z
A	0	0	A	0	0	B	0	1	0	0
B	0	1	A	0	0	C	1	0	0	0
C	1	0	A	0	0	C	1	0	0	1
D	1	1		d	d		d	d	d	d

Using Binary Encoding
for the State Assignment

Next state is a function
of the present state
and the input

Output is a function
of the present state
and the input
(Mealy Machine)

FSM Design Example 1 (Mealy)

6. Create state-assigned table
7. Select type of Flip-Flop to use

Present State			Next State				FF Inputs			
			w = 0		w = 1		w = 0		w = 1	
	Q_A	Q_B	Q_A^+	Q_B^+	Q_A^+	Q_B^+	D_A	D_B	D_A	D_B
A	0	0	0	0	0	1	0	0	0	1
B	0	1	0	0	1	0	0	0	1	0
C	1	0	0	0	1	0	0	0	1	0
D	1	1	d	d	d	d	d	d	d	d

FSM Design Example 1 (Mealy)

8. Determine Flip-Flop input equations and FSM output equation(s)

		$Q_A Q_B$			
		00	01	11	10
D_A	0	0	0	d	0
	1	0	1	d	1

		$Q_A Q_B$			
		00	01	11	10
D_B	0	0	0	d	0
	1	1	0	d	0

$$D_A = W \cdot Q_B + W \cdot Q_A$$

$$D_A = W \cdot (Q_A + Q_B)$$

$$D_B = W \cdot \overline{Q_A} \cdot \overline{Q_B}$$

		$Q_A Q_B$			
		00	01	11	10
Z	0	0	0	d	0
	1	0	0	d	1

$$Z = W \cdot Q_A$$


FSM Design Example 1 (Mealy)

9. Draw logic diagram

$$D_A = W(Q_A + Q_B)$$

$$D_B = W \cdot Q_A' \cdot Q_B'$$

$$Z=W.Q_A$$

 

FSM Design Example 1 (Mealy)

Q	Q^+	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Present State			Next State				FF Inputs							
			$w = 0$		$w = 1$		$w = 0$				$w = 1$			
	Q_A	Q_B	Q_A^+	Q_B^+	Q_A^+	Q_B^+	J_A	K_A	J_B	K_B	J_A	K_A	J_B	K_B
A	0	0	0	0	0	1	0	d	0	d	0	d	1	d
B	0	1	0	0	1	0	0	d	d	1	1	d	d	1
C	1	0	0	0	1	0	d	1	0	d	d	0	0	d
D	1	1	d	d	d	d	d	d	d	d	d	d	d	d

FSM Design Example 1 (Mealy)

J_A
 $Q_A Q_B$
 w

	00	01	11	10
0	0	0	d	d
1	0	1	d	d

$$J_A = w \cdot Q_B$$

K_A
 $Q_A Q_B$
 w

	00	01	11	10
0	d	d	d	1
1	d	d	d	0

$$K_A = \bar{w}$$

J_B
 $Q_A Q_B$
 w

	00	01	11	10
0	0	d	d	0
1	1	d	d	0


$$J_B = w \cdot \bar{Q}_A$$

K_B
 $Q_A Q_B$
 w

	00	01	11	10
0	d	1	d	d
1	d	1	d	d

$$K_B = 1$$

FSM Design Example 1 (Mealy)

 

FSM Design Example 2 (Mealy)


Design a Finite State Machine (FSM) that meets the following specifications:

1. The circuit has one input, w , and one output, z .
2. All changes in the circuit occur on the positive edge of the clock.
3. The output z is equal to 1 if the pattern 010 is detected on the input w . Otherwise, the value of z is equal to 0. Overlapping sequences should **not** be detected.

Input (w): 0 0 0 0 1 0 1 0 0 1 0 0 1 0 1 ...

Output (z): 0 0 0 0 0 1 0 0 0 0 1 0 0 1 0 ...

FSM Design Example 2 (Mealy)

 

FSM Design Example 3 (Mealy)


Design a Finite State Machine (FSM) that meets the following specifications:

1. The circuit has one input, w , and one output, z .
2. All changes in the circuit occur on the positive edge of the clock.
3. The output z is equal to 1 if the pattern 010 is detected on the input w . Otherwise, the value of z is equal to 0. Overlapping sequences **should** be detected.

Input (w): 0 0 0 0 1 0 1 0 0 1 0 0 1 0 1 ...



Output (z): 0 0 0 0 0 1 0 1 0 0 1 0 0 1 0 ...

FSM Design Example 3 (Mealy)

 


FSM Design Example 3 (Mealy)

Comparison:

  

FSM Design Example-1

Design a 3-bit counter

 

FSM Design Example

Present State			Next State		
A_2	A_1	A_0	A_2	A_1	A_0
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

FSM Design Example

<u>Present State</u>			<u>Next State</u>			<u>FF-Inputs</u>		
A2	A1	A0	A2+	A1+	A0+	TA2	TA1	TA0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

$Q(t)$	$Q(t + 1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

FSM Design Example

$A_2 \backslash A_1 A_0$		A_1			
		00	01	11	10
A_2	0	m_0	m_1	m_3 1	m_2
	1	m_4	m_5	m_7 1	m_6
		A_0			

$$T_{A2} = A_1 A_0$$

$A_2 \backslash A_1 A_0$		A_1			
		00	01	11	10
A_2	0	m_0	m_1 1	m_3 1	m_2
	1	m_4	m_5 1	m_7 1	m_6
		A_0			

$$T_{A1} = A_0$$

$A_2 \backslash A_1 A_0$		A_1			
		00	01	11	10
A_2	0	m_0 1	m_1 1	m_3 1	m_2 1
	1	m_4 1	m_5 1	m_7 1	m_6 1
		x			

$$T_{A0} = 1$$

FSM Design Example

TA0=1

TA1=A0

TA2=A0. A1

