

Course Name: Digital Hardware Design
Course Code: 17B1NEC741



Finite State Machine-7


Dr. Arti Noor

Dean, Academic Affairs

**Electronics and Communication Engineering,
Jaypee Institute of Information Technology, Noida**

Conversion From Mealy to Moore Machine

 
Example-1: Convert the following Mealy machine into an equivalent Moore machine



Present State	Next State 0		Next State 1	
	State	o/P	State	o/P
q₁	q₁	0	q₂	0
q₂	q₂	1	q₃	0
q₃	q₂	0	q₃	1

Conversion From Mealy to Moore Machine

 Example-1: Convert the following Mealy machine into an equivalent Moore machine



1. State q_1 has only one output. No Split
2. State q_2 and q_3 have both outputs 0 and 1. So create two states. For q_2 , two states will be q_{20} (with output 0) and q_{21} (with output 1).
3. Similarly, for q_3 two states will be q_{30} (with output 0) and q_{31} (with output 1).

Conversion From Mealy to Moore Machine

Example-1 : Design the Moore Machine from Mealy Machine

Present State	Next State 0		Next State 1	
	State	o/P	State	o/P
q_1	q_1	0	q_2	0
q_2	q_2	1	q_3	0
q_3	q_2	0	q_3	1

Mealy Machine State table

Present State	Next State 0	Next State 1	o/P
q_1	q_1	q_{20}	0
q_{20}	q_{21}	q_{30}	0
q_{21}	q_{21}	q_{30}	1
q_{30}	q_{20}	q_{31}	0
q_{31}	q_{20}	q_{31}	1


Moore Machine State table

Conversion From Mealy to Moore Machine

Example-1 : Design the Moore Machine from Mealy Machine

Present State	Next State 0	Next State 1	o/P
q_1	q_1	q_{20}	0
q_{20}	q_{21}	q_{30}	0
q_{21}	q_{21}	q_{30}	1
q_{30}	q_{20}	q_{31}	0
q_{31}	q_{20}	q_{31}	1

Moore Machine State table

 

FSM Optimization

State minimization

- Fewer states require fewer state bits.
- Fewer bits require fewer logic equations;

Encodings: state, inputs, outputs


- State encoding with fewer bits has fewer equations to implement.
 - However, each may be more complex.
- State encoding with more bits has simpler equations.
 - Complexity directly related to the complexity of the state diagram,
- Input/output encoding may or may not be under designer control

FSM Optimization by FSM Partitioning


Idea: Break a large FSM into two or more smaller FSMs

- ⇒ Less states in each partition
 - Simpler minimization and state assignment
 - Smaller combinational gates
 - Shorter critical path


Before

 

After

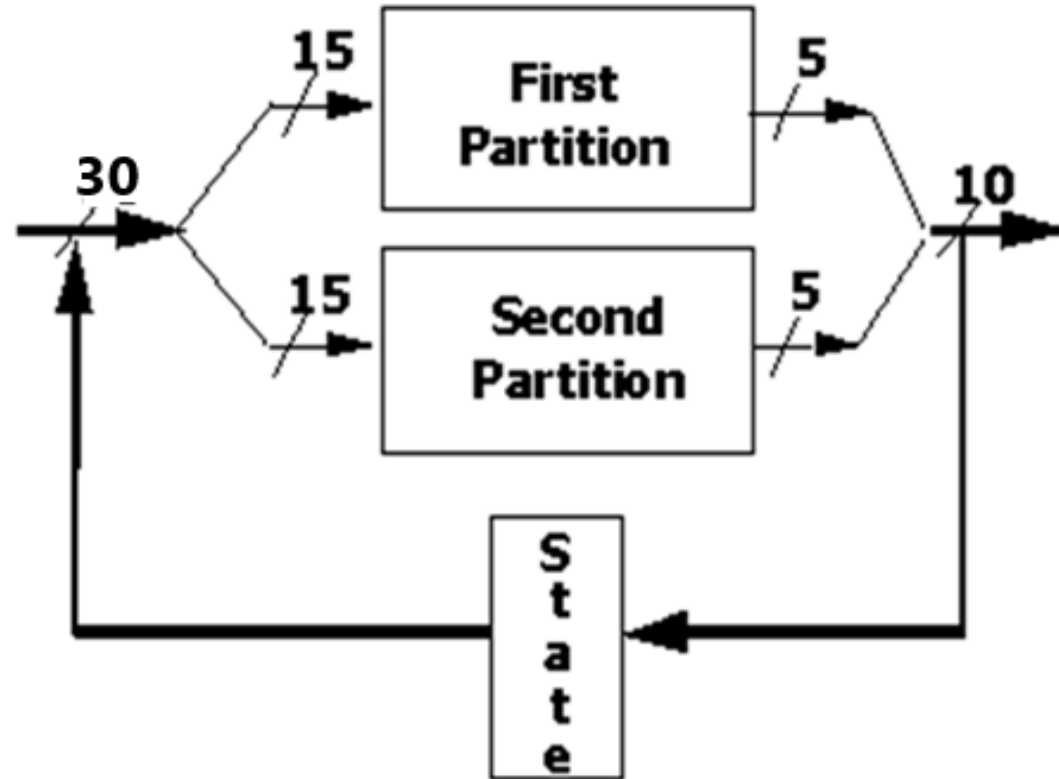


 Example: Partition this machine into two halves



Introduce idle states

 
- ◆ SA and SB handoff control between machines



Partitioning rules

Rule #1: Source-state transformation

Replace by transition to idle state (SA)

 

Rule #2: Destination state transformation


Replace with exit transition from idle state



Rule #3: Multiple transitions with same source or destination

Source \Rightarrow Replace by transitions to idle state (SA)

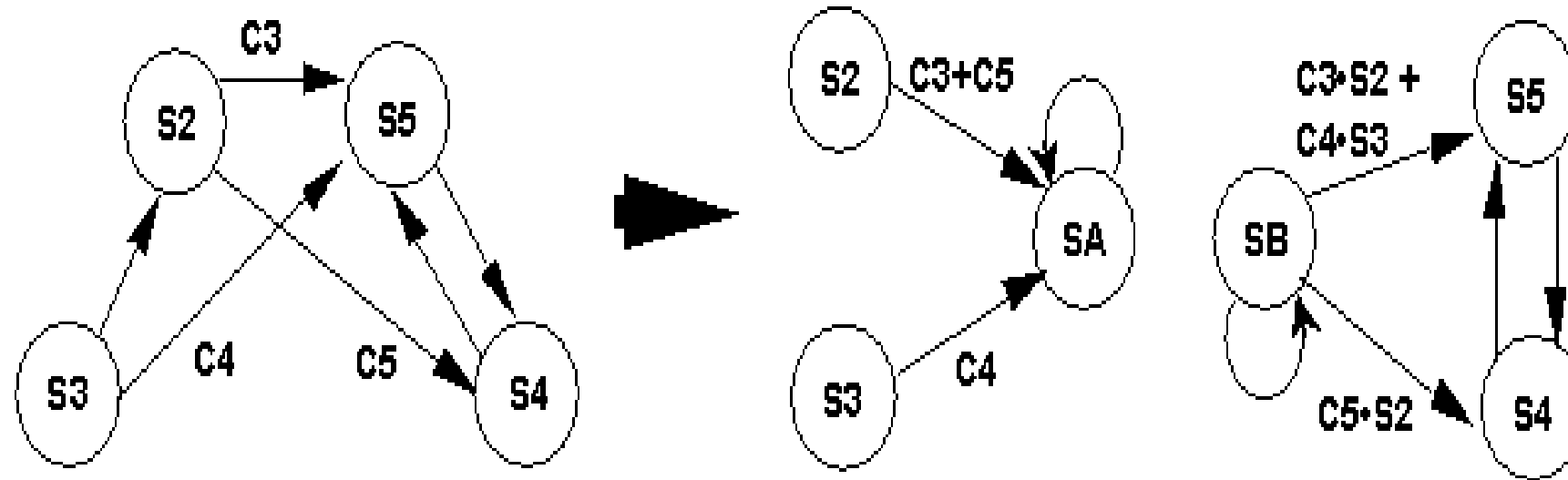Destination \Rightarrow Replace with exit transitions from idle state




Rule #4: Hold condition for idle state

OR exit conditions and invert



Example: Six-state up/down counter

Break into 2 parts

 


U \equiv count up

D \equiv count down

◆ Count sequence $S_0, S_1, S_2, S_3, S_4, S_5$

U \equiv count up
D \equiv count down

 

Up count



S_2 goes to S_A and holds, leaves after S_5

S_5 goes to S_B and holds, leaves after S_2

Down count


S_0 goes to S_A and holds, leaves after S_3

  S_3 goes to S_B and holds, leaves after S_0



Introduce idle states

- ◆ SA and SB handoff control between machines

 

Example 1: Partition the FSMs, one covering states S_0, S_1, S_2 and the other covering states S_3, S_4, S_5 . Show the labels of all transitions in your new machines.

