

Solution Tutorial 7

Ans 1

Characteristics Table of AB FF				Excitation Table of JK FF	
A	B	Q_n	Q_{n+1}	J	K
0	0	0	1	1	X
0	0	1	0	X	1
0	1	0	1	1	X
0	1	1	1	X	0
1	0	0	0	0	X
1	0	1	1	X	0
1	1	0	0	0	X
1	1	1	0	X	1

K-map for J


	BQ_n	00	01	11	10
A	0	1	X	X	1
	1	X	X		

$$J = A'$$

K-map for K

	BQ_n	00	01	11	10
A	0	X	1		X
	1	X		1	X

$$K = A'B' + AB$$

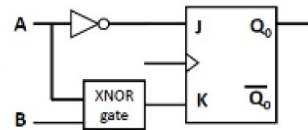

AB- FF using JK FF

Ans 2


D Flip Flop to J-K Flip Flop

Conversion Table

J-K Input		Outputs		D Input
J	K	Q_p	Q_{p+1}	
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

K-map


	KQ_p	00	01	11	10
J	0	0	1	0	0
	1	1	1	0	0
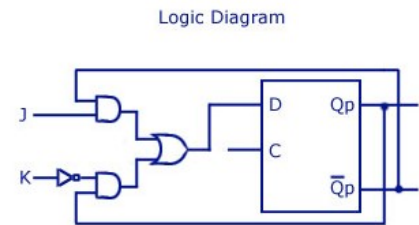
$$D = J\bar{Q}_p + \bar{K}Q_p$$


Ans 3

Assuming initial outputs (Q_0 , Q_1) are logic low (0). Since the FF's are working in toggle mode, therefore, the output waveforms of each flip flop are shown below.

Output frequency = $12 \text{ kHz}/4 = 3 \text{ kHz}$.

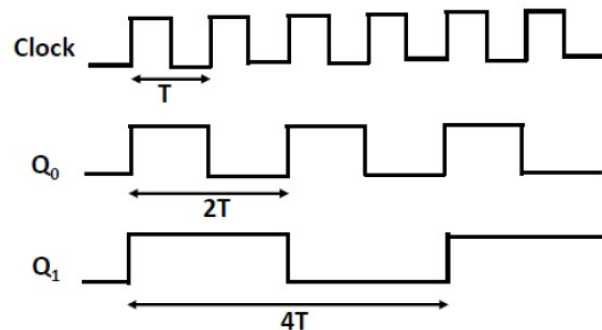

Ans 4


T	$D = T \oplus Q$	$Q +$
0	Q	Q
1	\bar{Q}	\bar{Q}

} Toggle action.

Ans 5

Q	$J = \bar{Q}$	K	$Q +$	
0	1	1	1	After 1st pulse
1	0	1	0	After 2nd pulse
0	1	1	1	After 3rd pulse
1	0	1	0	After 4th pulse
0	1	1	1	After 5th pulse
1	0	1	0	After 6th pulse.

Ans 6

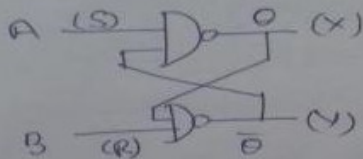


$A = B = 1$
 B - Replaced by 101010---

	A	B	Out
Initially	1	1	On
Now if $B \Rightarrow$		0	
		1	
		0	
		1	
		0	

i.e. for $A=B=1$, outputs X, Y will remain same after applying CLK pulse

i.e. Now $X=0, Y=1$ will remain fixed

Ans 7

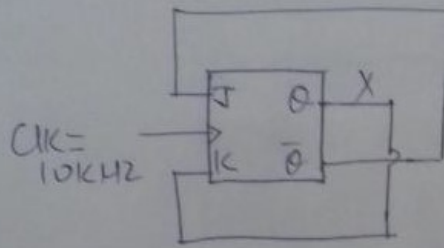

Let initially $Q=0$, i.e. $X=0$
So $\bar{Q}=1$

then $J=1$, $K=0$

after triggering 1st clk, $Q=X=1$
 $\bar{Q}=0$

$\underline{J}=\underline{\bar{Q}}=0$, $\underline{K}=X=1$

after triggering 2nd clk, $Q=0$
 $\bar{Q}=1$

(which is same as the initial value)

i.e. Q, \bar{Q} repeats after 2 clk pulses.

\Rightarrow output freq. at $X = \frac{10\text{kHz}}{2} = 5\text{kHz}$