

Course Name: Digital Hardware Design
Course Code: 17B1NEC741











Finite State Machine-4

Dr. Arti Noor

Dean, Academic Affairs

**Electronics and Communication Engineering,
Jaypee Institute of Information Technology, Noida**

Sequential Storage Units

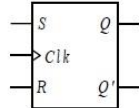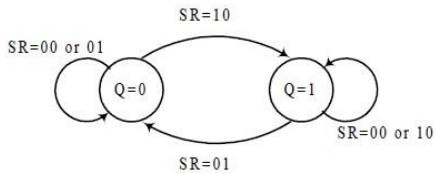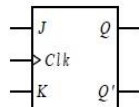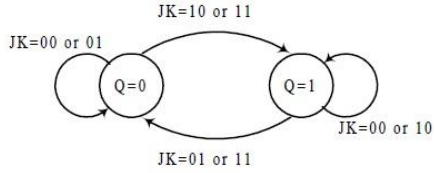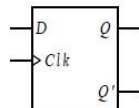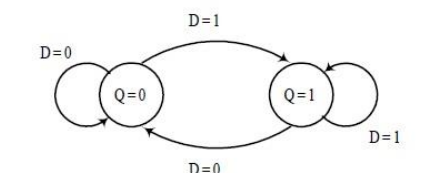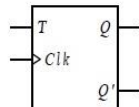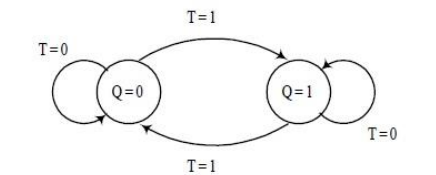
Name / Symbol	Characteristic (Truth) Table	State Diagram / Characteristic Equations	Excitation Table																																																								
<div>SR</div> <div></div>	<table><tr><th>S</th><th>R</th><th>Q</th><th>Q_{next}</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>×</td></tr><tr><td>1</td><td>1</td><td>1</td><td>×</td></tr></table>	S	R	Q	Q _{next}	0	0	0	0	0	0	1	1	0	1	0	0	0	1	1	0	1	0	0	1	1	0	1	1	1	1	0	×	1	1	1	×	<div></div> <div>$Q_{next} = S + R'Q$$SR = 0$</div>	<table><tr><th>Q</th><th>Q_{next}</th><th>S</th><th>R</th></tr><tr><td>0</td><td>0</td><td>0</td><td>×</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>×</td><td>0</td></tr></table>	Q	Q _{next}	S	R	0	0	0	×	0	1	1	0	1	0	0	1	1	1	×	0
S	R	Q	Q _{next}																																																								
0	0	0	0																																																								
0	0	1	1																																																								
0	1	0	0																																																								
0	1	1	0																																																								
1	0	0	1																																																								
1	0	1	1																																																								
1	1	0	×																																																								
1	1	1	×																																																								
Q	Q _{next}	S	R																																																								
0	0	0	×																																																								
0	1	1	0																																																								
1	0	0	1																																																								
1	1	×	0																																																								
<div>JK</div> <div></div>	<table><tr><th>J</th><th>K</th><th>Q</th><th>Q_{next}</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table>	J	K	Q	Q _{next}	0	0	0	0	0	0	1	1	0	1	0	0	0	1	1	0	1	0	0	1	1	0	1	1	1	1	0	1	1	1	1	0	<div></div> <div>$Q_{next} = J'K'Q + JK' + JKQ'$$= J'K'Q + JK'Q + JK'Q' + JKQ'$$= K'Q(J' + J) + JQ'(K' + K)$$= K'Q + JQ'$</div>	<table><tr><th>Q</th><th>Q_{next}</th><th>J</th><th>K</th></tr><tr><td>0</td><td>0</td><td>0</td><td>×</td></tr><tr><td>0</td><td>1</td><td>1</td><td>×</td></tr><tr><td>1</td><td>0</td><td>×</td><td>1</td></tr><tr><td>1</td><td>1</td><td>×</td><td>0</td></tr></table>	Q	Q _{next}	J	K	0	0	0	×	0	1	1	×	1	0	×	1	1	1	×	0
J	K	Q	Q _{next}																																																								
0	0	0	0																																																								
0	0	1	1																																																								
0	1	0	0																																																								
0	1	1	0																																																								
1	0	0	1																																																								
1	0	1	1																																																								
1	1	0	1																																																								
1	1	1	0																																																								
Q	Q _{next}	J	K																																																								
0	0	0	×																																																								
0	1	1	×																																																								
1	0	×	1																																																								
1	1	×	0																																																								
<div>D</div> <div></div>	<table><tr><th>D</th><th>Q</th><th>Q_{next}</th></tr><tr><td>0</td><td>×</td><td>0</td></tr><tr><td>1</td><td>×</td><td>1</td></tr></table>	D	Q	Q _{next}	0	×	0	1	×	1	<div></div> <div>$Q_{next} = D$</div>	<table><tr><th>Q</th><th>Q_{next}</th><th>D</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	Q	Q _{next}	D	0	0	0	0	1	1	1	0	0	1	1	1																																
D	Q	Q _{next}																																																									
0	×	0																																																									
1	×	1																																																									
Q	Q _{next}	D																																																									
0	0	0																																																									
0	1	1																																																									
1	0	0																																																									
1	1	1																																																									
<div>T</div> <div></div>	<table><tr><th>T</th><th>Q</th><th>Q_{next}</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	T	Q	Q _{next}	0	0	0	0	1	1	1	0	1	1	1	0	<div></div> <div>$Q_{next} = TQ' + T'Q = T \oplus Q$</div>	<table><tr><th>Q</th><th>Q_{next}</th><th>T</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	Q	Q _{next}	T	0	0	0	0	1	1	1	0	1	1	1	0																										
T	Q	Q _{next}																																																									
0	0	0																																																									
0	1	1																																																									
1	0	1																																																									
1	1	0																																																									
Q	Q _{next}	T																																																									
0	0	0																																																									
0	1	1																																																									
1	0	1																																																									
1	1	0																																																									

FSM Design Example-2

A vending machine will open the door to let out a pack of gum if it receives 15 cents or more in denominations of 5 (Dime) and 10 (Nickel) cents. Consider one input at a time. No return.

Input Sequence:

 1. 3 Dimes(15)
2. 2 Dimes & Nickel(20)
3. Dime, Nickle(15)
4. Nickle, Dime(15)
5. 2 Nickles (20)



FSM Design Example-2

[illegible]

State Assignment

- Some state assignments are better than others.
- The state assignment influences the complexity of the state machine.
 - The combinational logic required in the state machine design is dependent on the state assignment.
- Types of state assignment
 - Binary encoding
 - Gray-code encoding
 - One-hot encoding

Example


Design a FSM that detects a sequence of two or more consecutive ones on an input bit stream.

The FSM should output a 1 when the sequence is detected, and a 0 otherwise.

Input: 0 1 1 1 0 1 0 1 1 0 1 1 1 0 1 ...

Output: 0 0 1 1 0 0 0 0 1 0 0 1 1 0 0 ...

Example

 

State
Diagram

Example: State Assignment 1

Present State			Next State						Output
			w = 0			w = 1			
	Q_A	Q_B		Q_A^+	Q_B^+		Q_A^+	Q_B^+	z
S_0	0	0	S_0	0	0	S_1	0	1	0
S_1	0	1	S_0	0	0	S_2	1	0	0
S_2	1	0	S_0	0	0	S_2	1	0	1
	1	1		d	d		d	d	d

Using Binary Encoding
for the State Assignment

Example: State Assignment 1

Present State			Next State				FF Inputs			
			w = 0		w = 1		w = 0		w = 1	
	Q_A	Q_B	Q_A^+	Q_B^+	Q_A^+	Q_B^+	D_A	D_B	D_A	D_B
S_0	0	0	0	0	0	1	0	0	0	1
S_1	0	1	0	0	1	0	0	0	1	0
S_2	1	0	0	0	1	0	0	0	1	0
	1	1	d	d	d	d	d	d	d	d

Characteristic Equation: $D = Q^+$

Example: State Assignment 1

		$Q_A Q_B$			
		00	01	11	10
D_A	W	0	0	d	0
	1	0	1	d	1

$$D_A = W \cdot Q_B + W \cdot Q_A$$

$$D_A = W \cdot (Q_A + Q_B)$$


		$Q_A Q_B$			
		00	01	11	10
D_B	W	0	0	d	0
	1	1	0	d	0

$$D_B = W \cdot \overline{Q_A} \cdot \overline{Q_B}$$

		Q_A	
		0	1
Z	Q_B	0	1
	1	0	d

$$Z = Q_A$$

Example: State Assignment 1

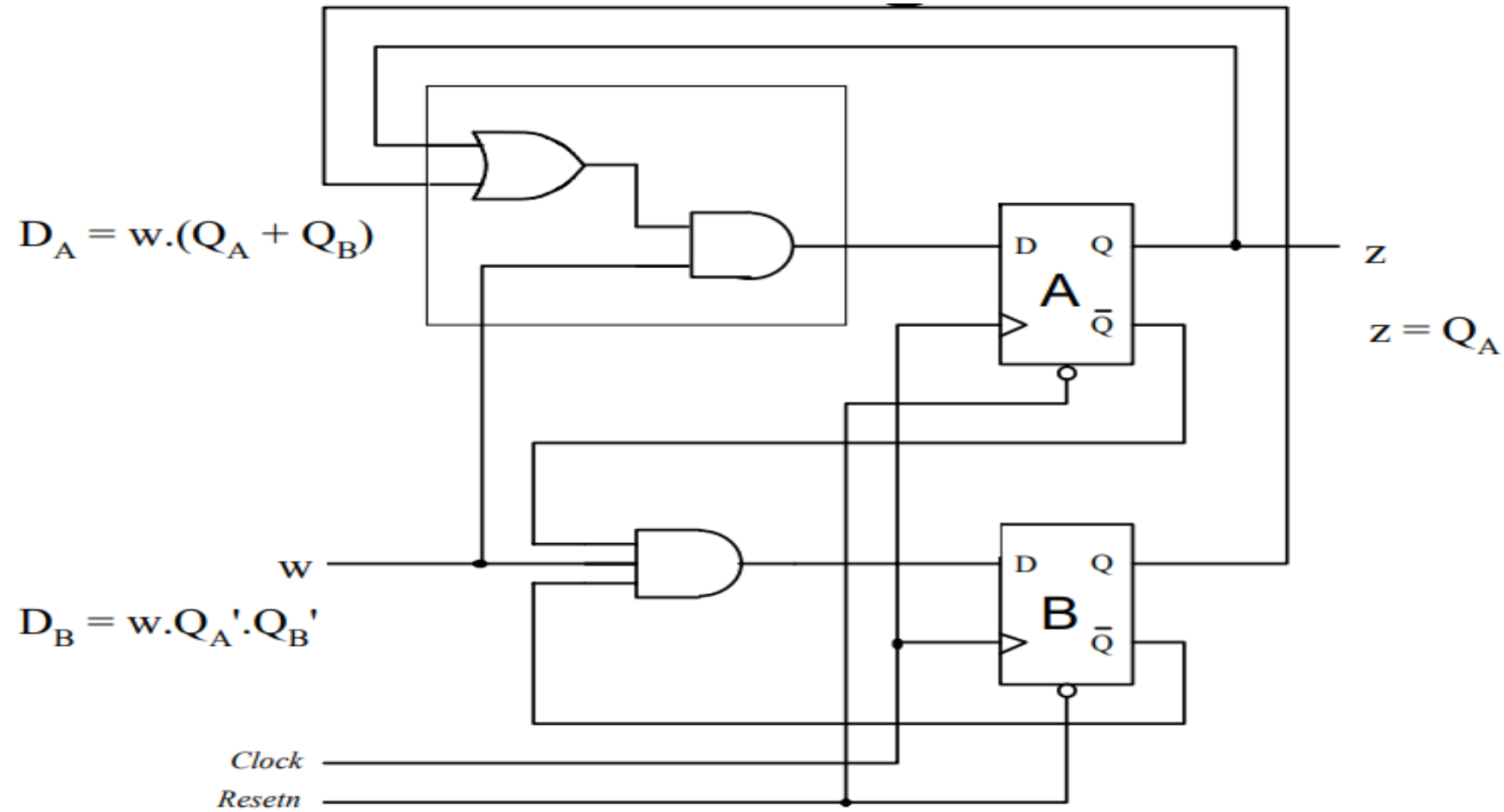


Example: State Assignment 2

Gray code consists of a sequence where only one bit changes between one value and the next. In addition to also using the minimum number of bits, this encoding minimizes dynamic power consumption if the sequence of states is followed optimally.

Example: State Assignment 2

n-bit Gray Code

 

Present State			Next State						Output
			w = 0			w = 1			
	Q _A	Q _B		Q _A ⁺	Q _B ⁺		Q _A ⁺	Q _B ⁺	z
S ₀	0	0	S ₀	0	0	S ₁	0	1	0
S ₁	0	1	S ₀	0	0	S ₂	1	1	0
S ₂	1	1	S ₀	0	0	S ₂	1	1	1
	1	0		d	d		d	d	d

Using Gray-code Encoding
for the State Assignment

Example: State Assignment 2

Present State			Next State				FF Inputs			
			w = 0		w = 1		w = 0		w = 1	
	Q_A	Q_B	Q_A^+	Q_B^+	Q_A^+	Q_B^+	D_A	D_B	D_A	D_B
S_0	0	0	0	0	0	1	0	0	0	1
S_1	0	1	0	0	1	1	0	0	1	1
S_2	1	1	0	0	1	1	0	0	1	1
	1	0	d	d	d	d	d	d	d	d

Characteristic Equation: $D = Q^+$

Example: State Assignment 2

D_A

 w

 $Q_A Q_B$

	00	01	11	10
0	0	0	0	d
1	0	1	1	d

$$D_A = w \cdot Q_B$$

D_B

 w

 $Q_A Q_B$

	00	01	11	10
0	0	0	0	d
1	1	1	1	d

$$D_B = w$$

z


 Q_A

 Q_B


	0	1
0	0	d
1	0	1

$$z = Q_A$$

Example: State Assignment 2

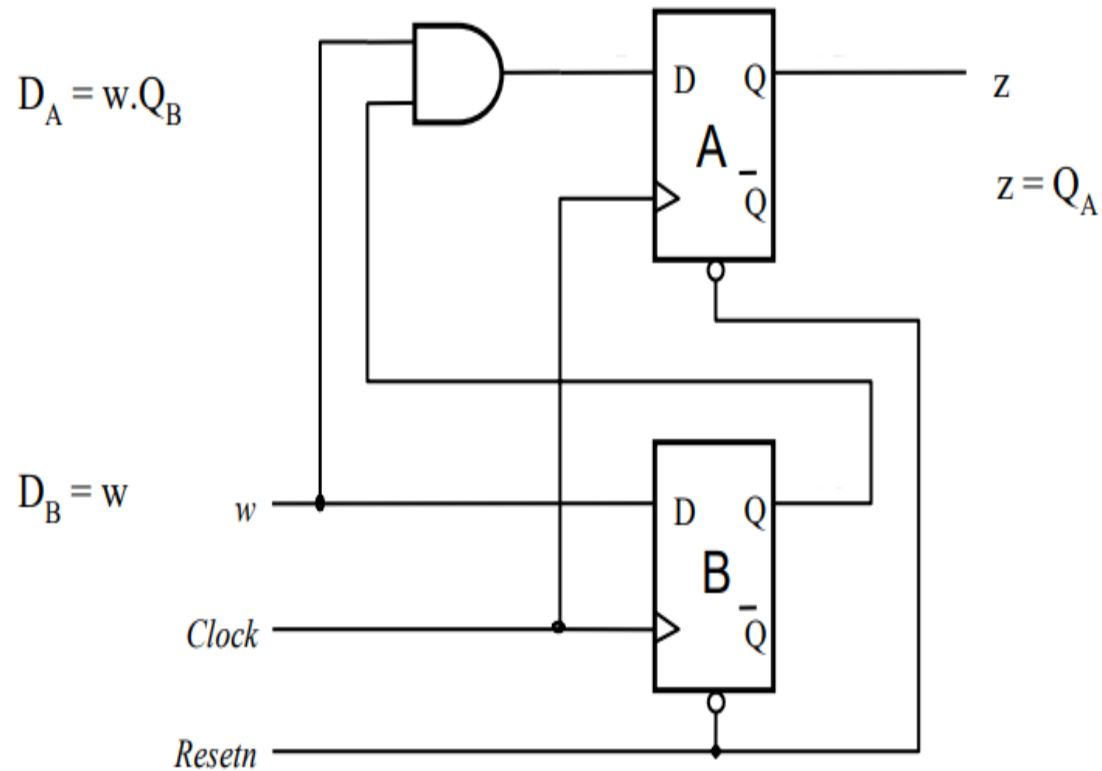

Gray Code

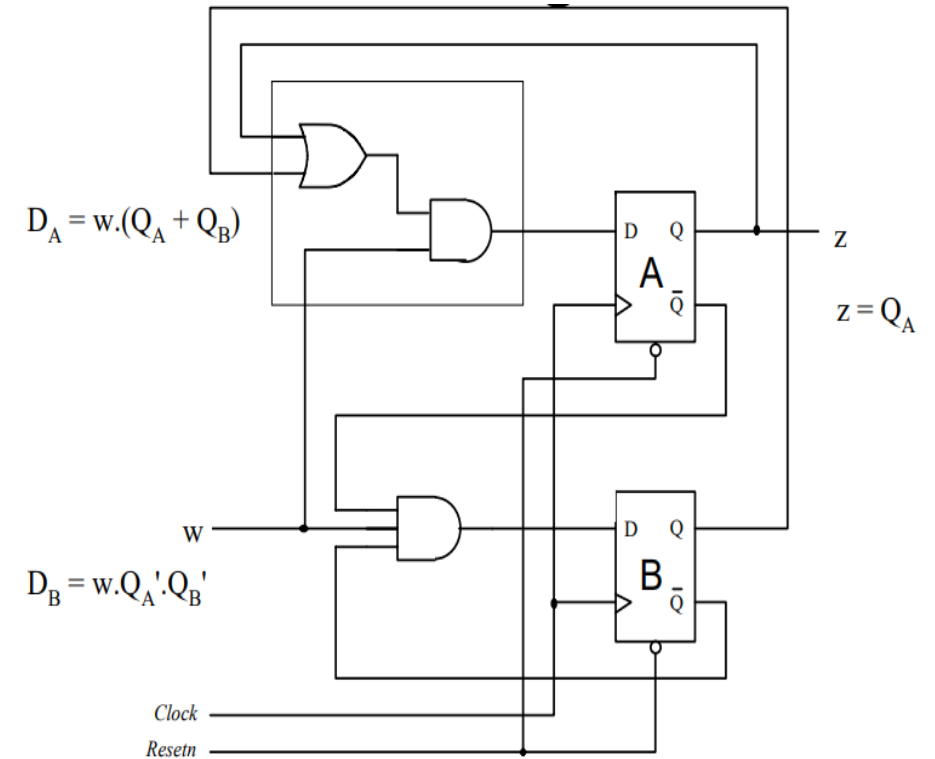

Binary Code

Example: State Assignment 3

One-Hot coding

- Encode n states using n flip-flops.
- Assign a single “1” for each state. Example: 0001 0010 0100 1000.
- Propagate a single “1” from one flip-flop to the next .All other flip-flop outputs are “0”

Example: State Assignment 3

Present State				Next State							
				w = 0				w = 1			
	Q_A	Q_B	Q_C		Q_A^+	Q_B^+	Q_C^+		Q_A^+	Q_B^+	Q_C^+
S_0	0	0	1	S_0	0	0	1	S_1	0	1	0
S_1	0	1	0	S_0	0	0	1	S_2	1	0	0
S_2	1	0	0	S_0	0	0	1	S_2	1	0	0

Using One-hot Encoding
for the State Assignment

For each state only one flip-flop is set to 1.
The remaining combination of state variables are not used.

Characteristic Equation: $D = Q^+$

Example: State Assignment 3

D_A

$Q_B Q_C$	00	01	11	10
$w Q_A$				
00	d	0	d	0
01	0	d	d	d
11	1	d	d	d
10	d	0	d	1

$$D_A = w \cdot \bar{Q}_C$$

D_B

$Q_B Q_C$	00	01	11	10
$w Q_A$				
00	d	0	d	0
01	0	d	d	d
11	0	d	d	d
10	d	1	d	0


$$D_B = w \cdot Q_C$$

D_C

$Q_B Q_C$	00	01	11	10
$w Q_A$				
00	d	1	d	1
01	1	d	d	d
11	0	d	d	d
10	d	0	d	0

$$D_C = \bar{w}$$

Example: State Assignment 3

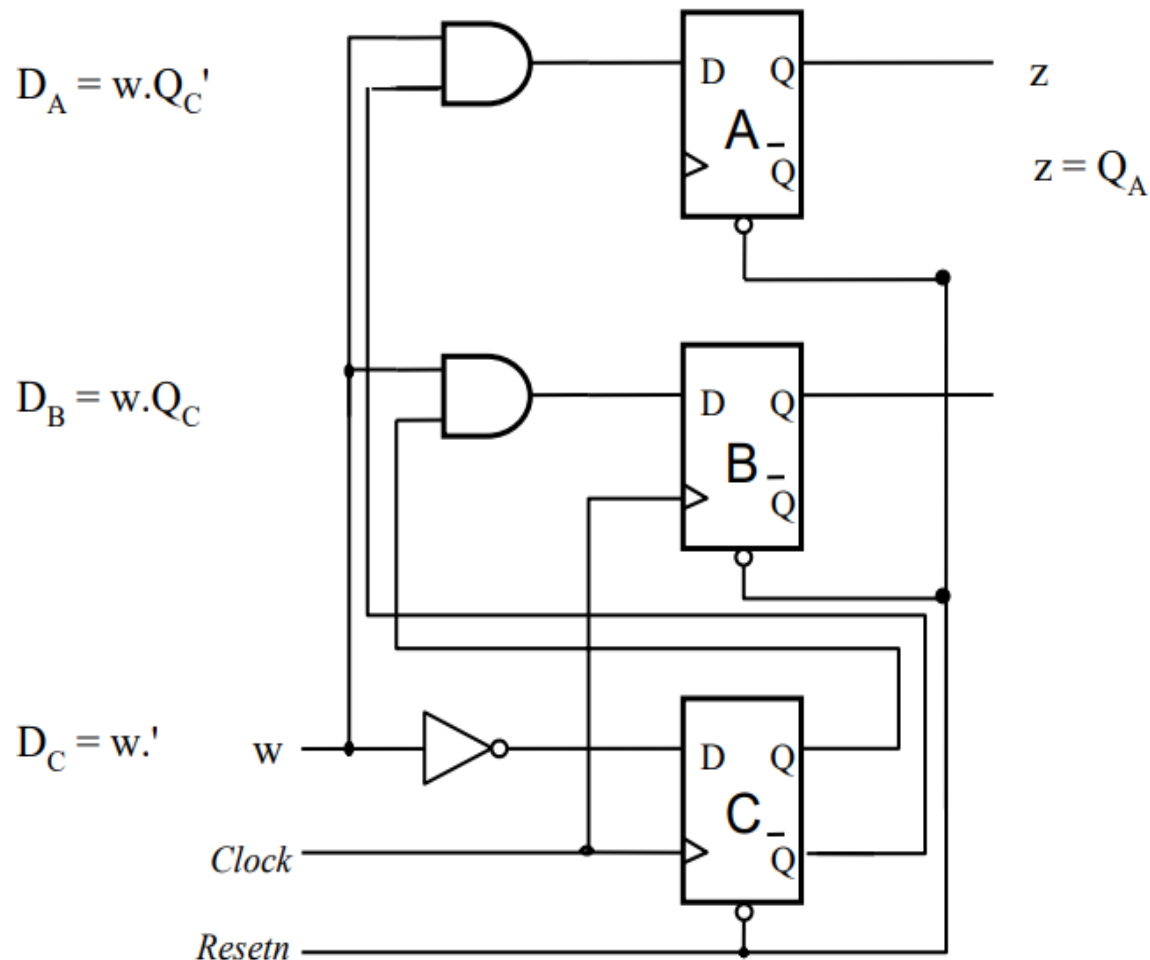

- This may not seem very efficient at first because of the number of bits used, and the excessive number of invalid states.
- However, one-hot encoding is very good at simplifying the stimulus logic for the flip flops because there's no need to decode the states. The bits are the states.