

Course Name: Digital Hardware Design
Course Code: 17B1NEC741



Clock Dividers

Dr. Arti Noor
Dean, Academic Affairs
Electronics and Communication Engineering,
Jaypee Institute of Information Technology, Noida

Introduction


- Sequential circuits need a reliable clock signal for circuit operations.
- Digital systems need several different clock signals to drive different subsystems.
- Cock divider circuit creates different frequency clock signals from an input clock source.

Clock Frequency Dividers for f/n in three cases:

- Where n is an odd integer number
- Where n is even integer number
- Where n is a decimal number

Frequency Divider for f/n : odd number

Example $n=3$

 


$$T_{\text{out}} = N T_{\text{in}}$$

$$F = 1/T$$

For $N=3$

$$T_{\text{out}} = 3 T_{\text{in}}$$

 


Requirement:

1. Mod N counter
2. DFFs
3. And some Logic


Frequency Divider for f/n : odd number

Example $n=3$

DFF

 

 Q is delayed by T for +clk edge
Q is delayed by $T/2$ for -clk edge



T

Mod 3 counter

- It can be constructed by using 2 FF(2^2) because FF required for mod 3 counter.
- The no. of states required for mod counter is three states 00, 01, 10 and the final state is xx.

MSB	LSB	Decimal value
0	0	0
0	1	1
1	0	2
x	x	x

Clock divide by 3

- A divide by 3 clock requires a mod 3 counter.
- It can be constructed by using 2 FF(2^2) because FF required for mod 3 counter.
- The no. of states required for mod counter is three states 00, 01, 10 and the final state is xx.
- The output of the clock divide by three is not 50% duty cycle. The duty cycle will be 75% if the output is 1,1,0

Current state		Next state		Output
Qb	Qa	Qb+	Qa+	
0	0	0	1	1
0	1	1	0	1
1	0	0	0	0
x	x	x	x	x

Clock divide by 3

The K-Map realization for input FFA

Qb \ Qa	0	1
0	1	0
1	0	x

$$Da = Qa'Qb'$$

The K-Map realization for input FFB

Qb \ Qa	0	1
0	0	0
1	1	x

$$Db = Qa$$

The K-Map realization for output of the FFB


Qb \ Qa	0	1
0	1	0
1	1	x

AN-DHD-Pul-Gen-4-JIIT

$$Out = Qa + Qb'$$


Clock divide by 3

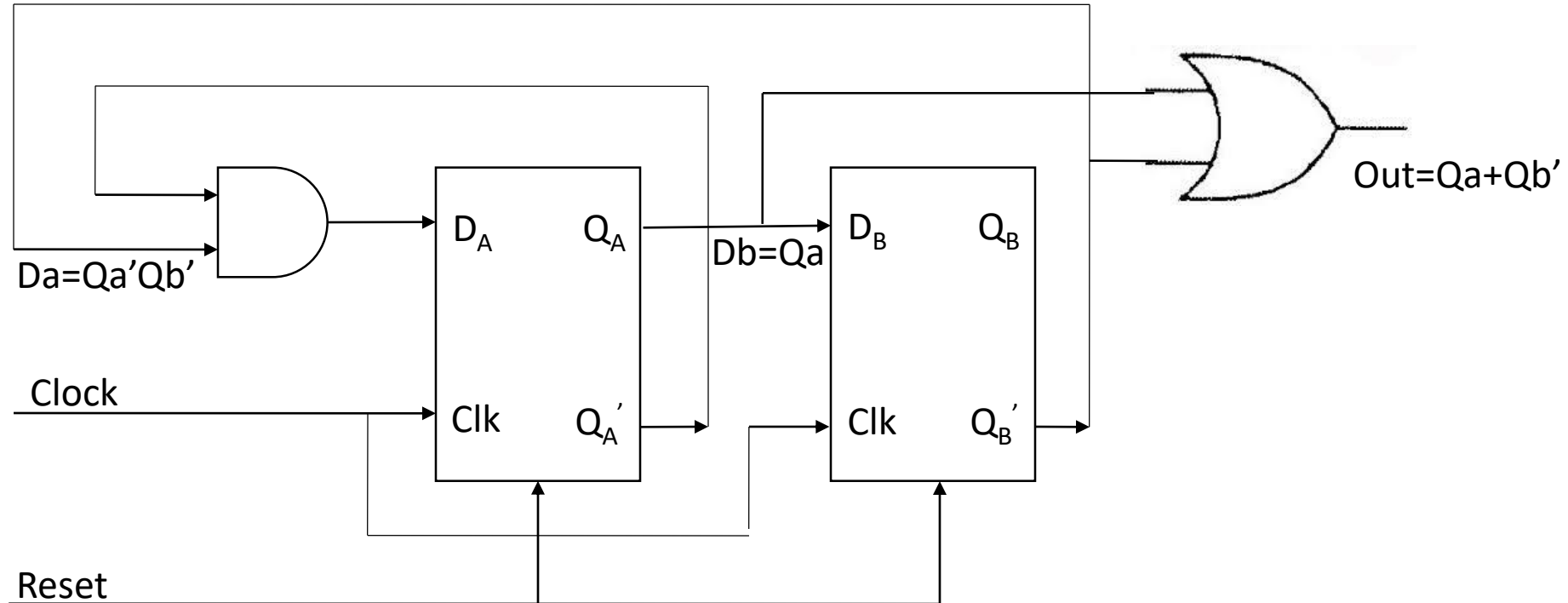- The micro architecture of the clock divide by 3 is



Clock divide by 3

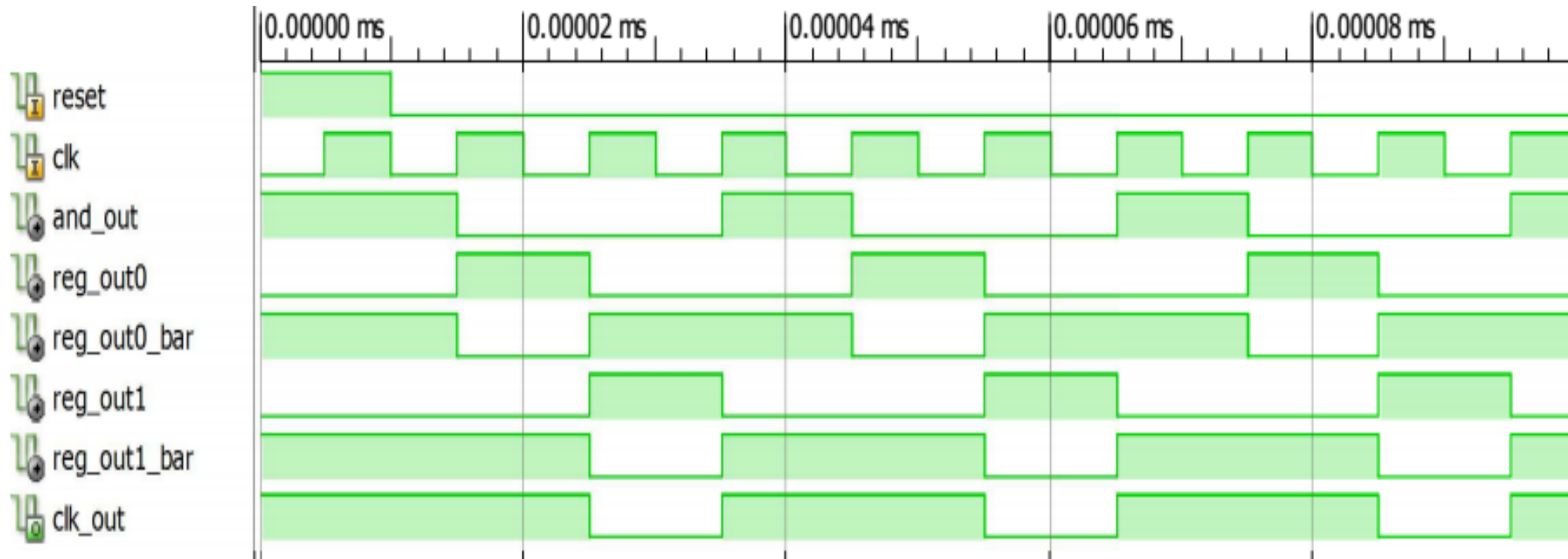- Timing diagram for clock divided by 3 without 50% duty cycle




Input : Clock and reset

Output : clk_out


Clock divide by 3

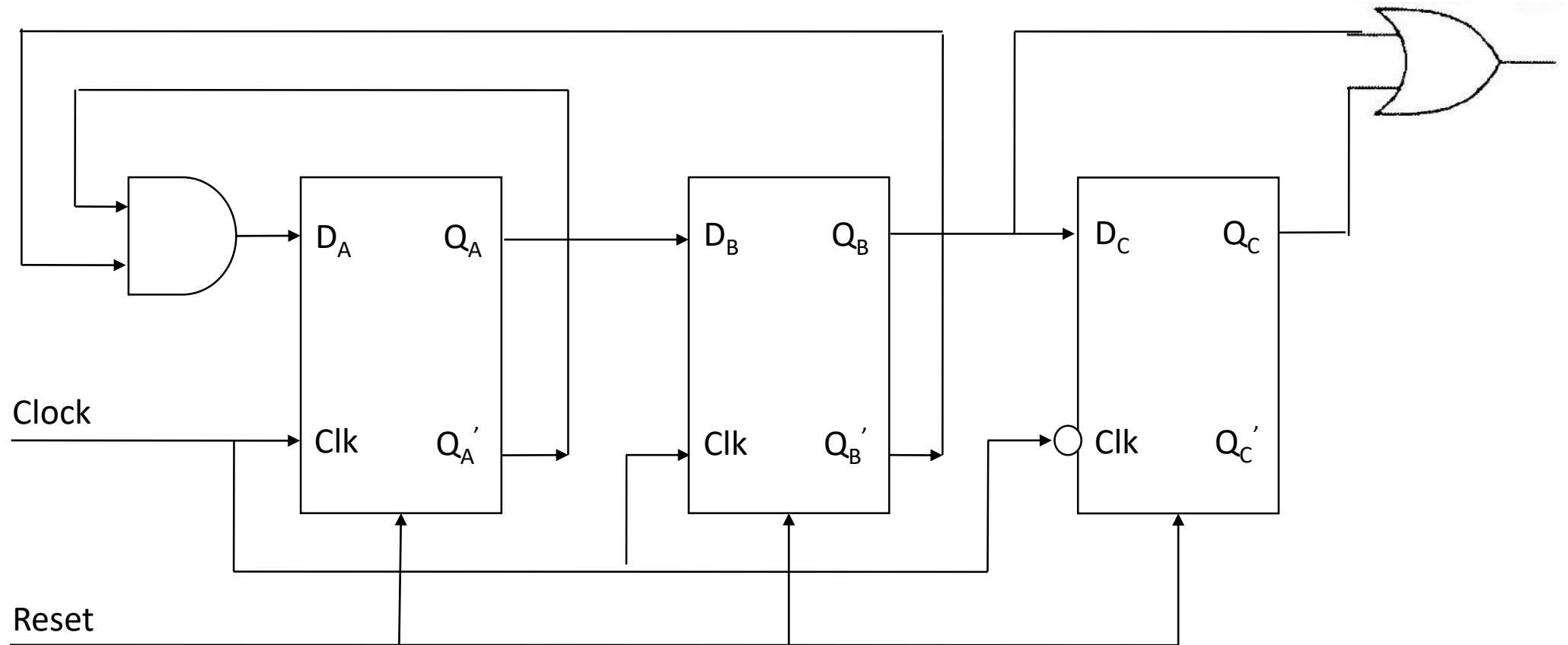- To get 50% duty cycle the out of the FFB will as input to the negative edge trigger FF.
- The output of the third FF and the output of the second FF is given as input to the OR gate.



Clock divided by 3

 
Timing diagram for clock divided by 3 with 50% duty cycle.




Input : Clock and reset

Output : clk_out


Generic Circuit for Clock divided by 3

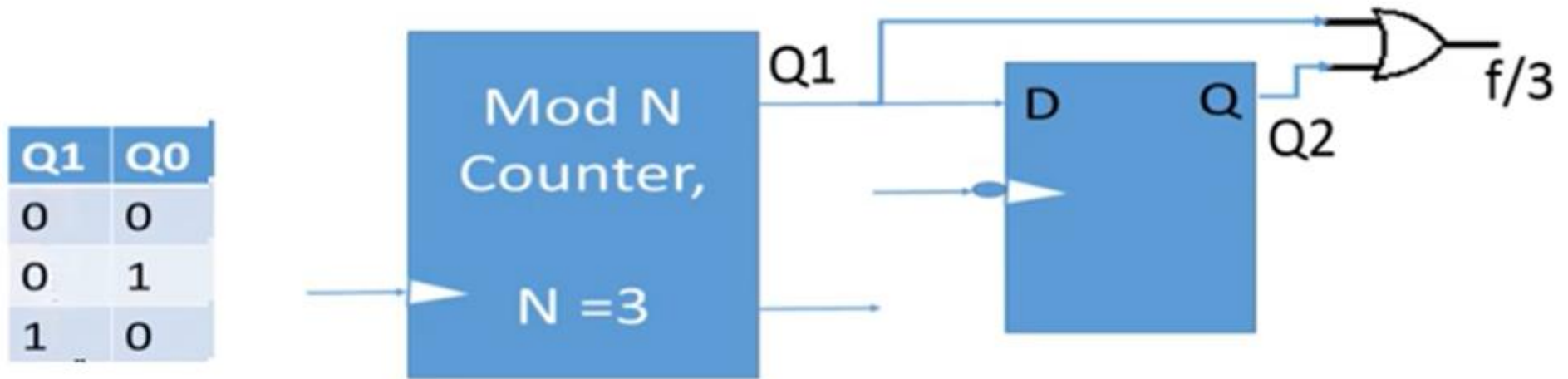

Frequency Divider for $f/3$

 


$Q1$	$Q0$
0	0
0	1
1	0

 

Clock divider by 5


Frequency Divider for $f/5$ and Duty Cycle 50%

Q2	Q1	Q0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0

 

Clock divider by 5

Q2	Q1	Q0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0

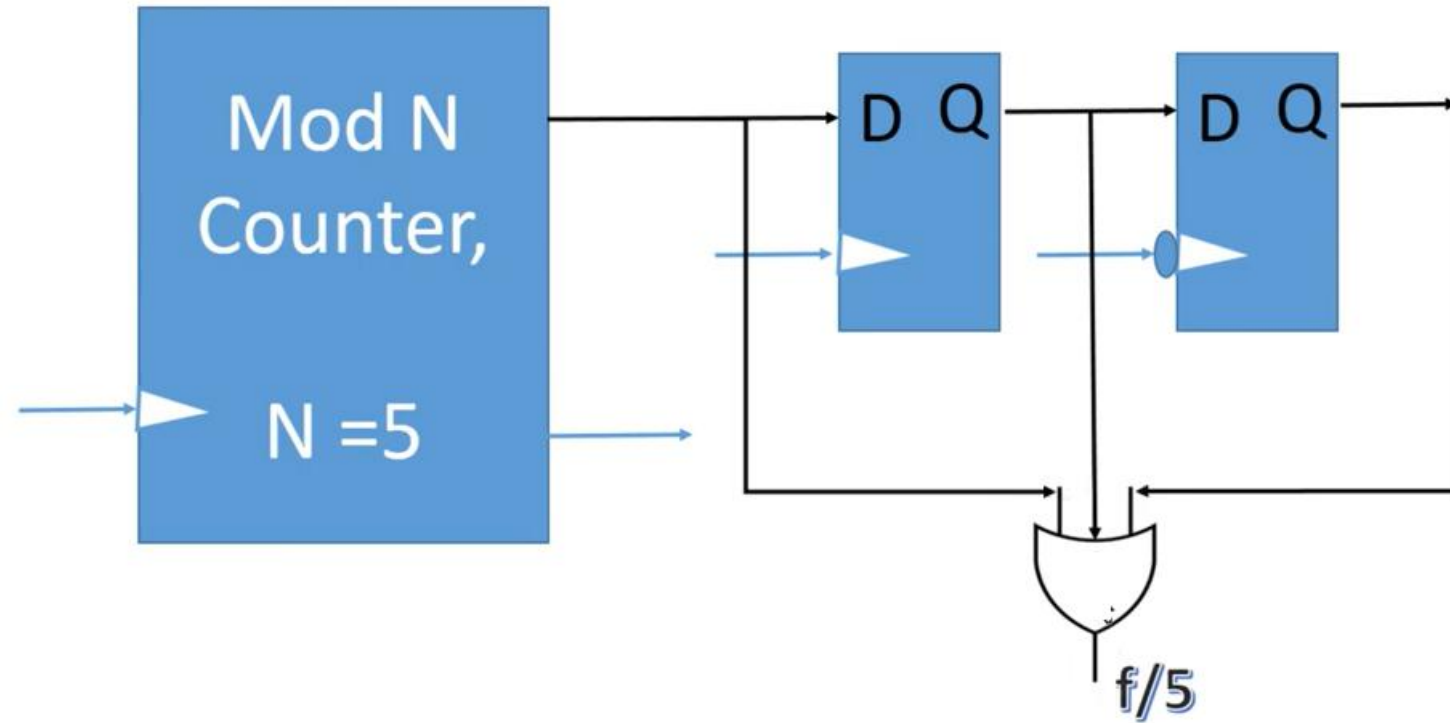

Clock divider by 5

Alternative Method


Frequency Divider for $f/5$ and Duty Cycle 50%

Optimization

Pass the output of the second FF to one more FF which is triggered with negedge of clk
then make ORing of these two.

Q2	Q1	Q0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0

It is High for 2 cycle & low for 3 cycle

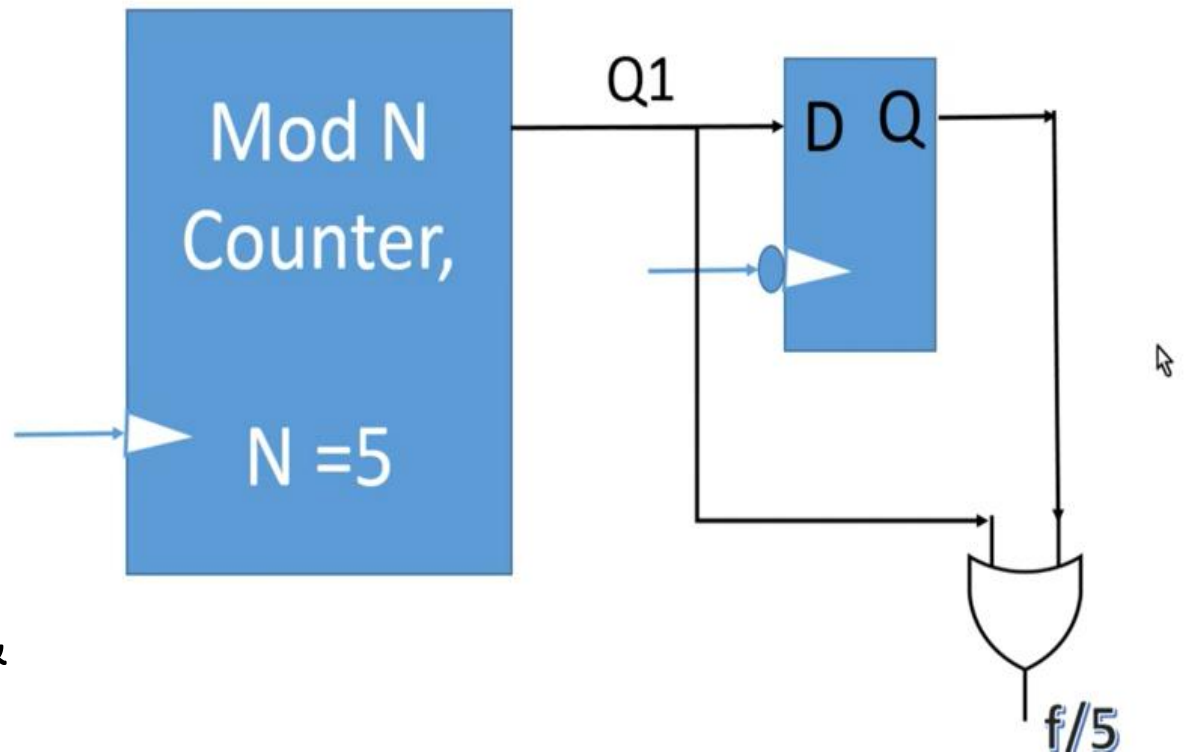


Conclusion for implementation of f/n divider

- Need to include ModN Counter
- Positive edge triggered flip flop alters output by 1 clock cycle.
- Negative edge trigger flip flop alters output by $\frac{1}{2}$ clock cycle.
- Need to choose one of the output of ModN counter having frequency f/n and less alteration required for hardware optimization.

Frequency Divider for $f/7$ and Duty Cycle 50%


Optimization

Q2	Q1	Q0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0

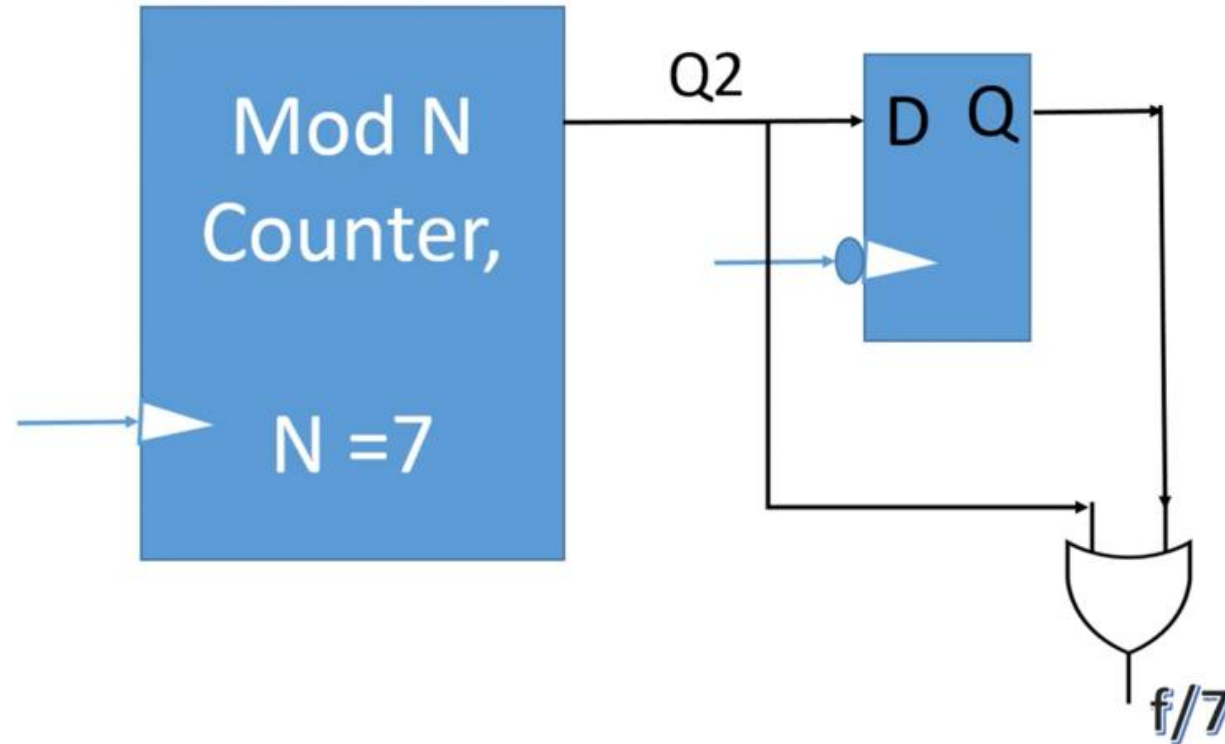


Frequency Divider for f/n , where n is an even number

 
Let us consider the easiest case, $n = 2$






Expected waveform

 


Frequency Divider for $f/2$

 


Q_0
0
1

 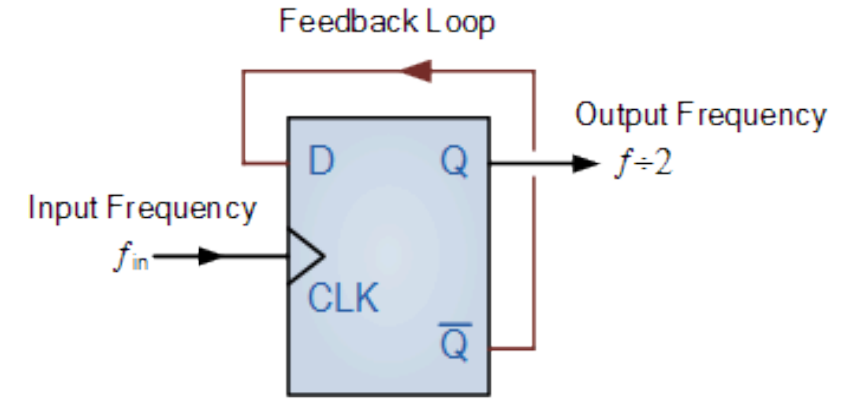 


Frequency Divider for $f/4$

 

Q1	Q0
0	0
0	1
1	0
1	1

 


Frequency Divide by 4 ($f/4$)

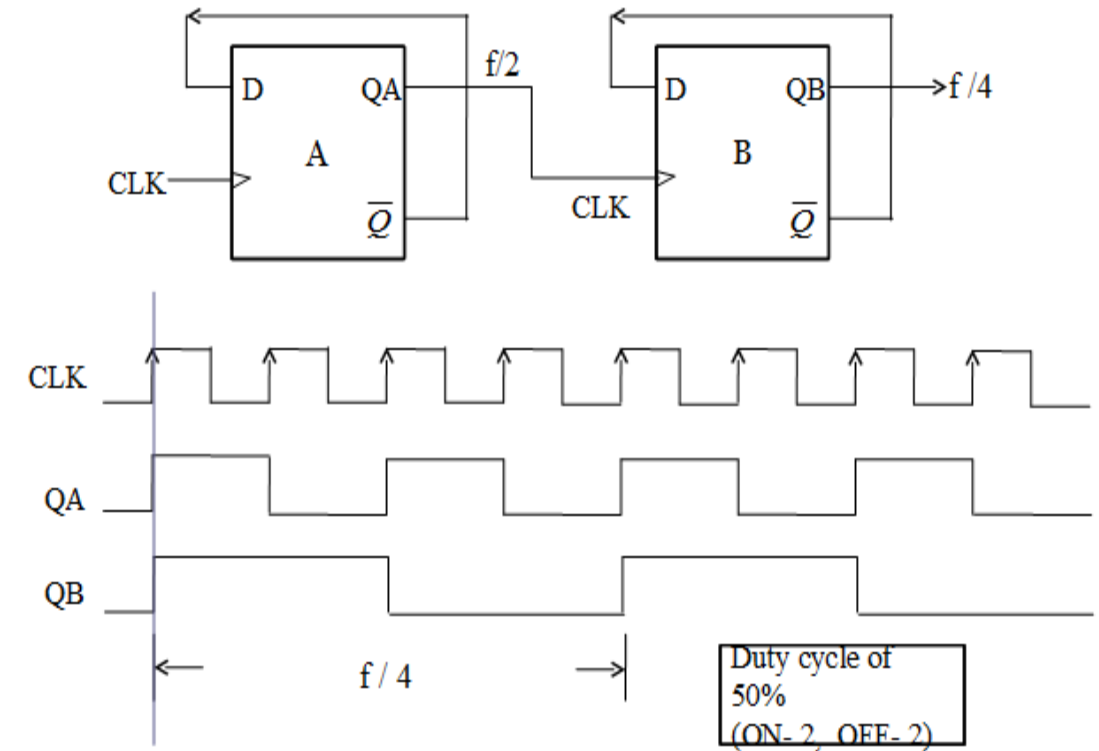


Frequency Divider for $f/6$


Q2	Q1	Q0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1

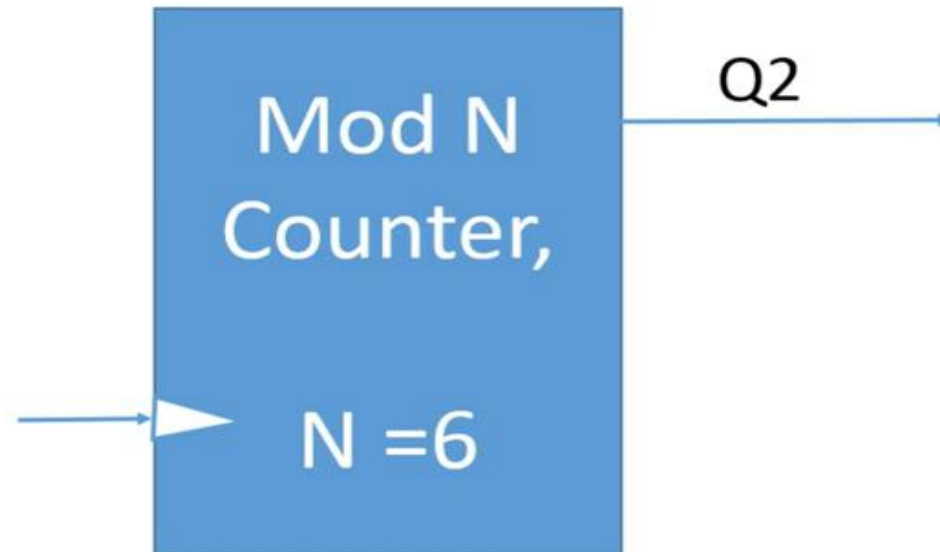

Frequency Divider for $f/6$

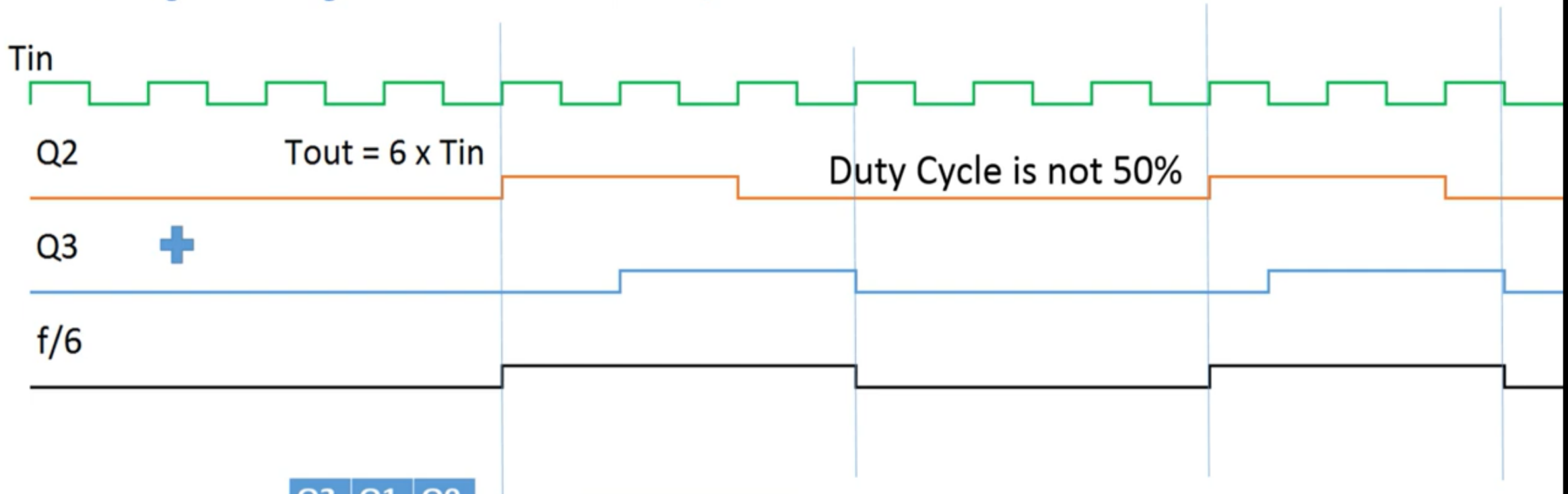


Q2	Q1	Q0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1

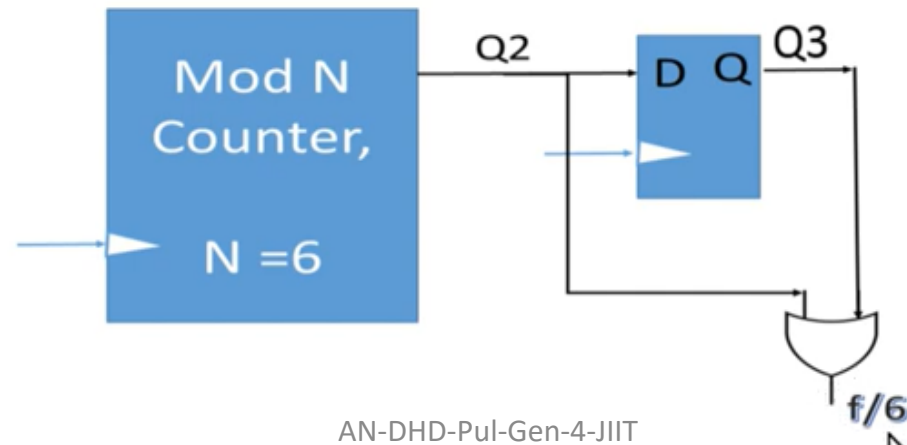


Frequency Divider for f/n , where n is a fraction

 Let us consider the easiest case, $n = 1.5$



Expected waveform

 

Clock
Divider
 F/n
 n is integer

Flip Flop
Work at
Both
Edges


$$T_1 = 3T \text{ so } 1/F_1 = 3/f$$

$$F_1 = f/3$$


Similarly

$$T_2 = T_1/2$$


 
$$\text{So } F_2 = 2F_1 = 2*f/3 = f/1.5$$





Frequency Divider for $f/1.5$

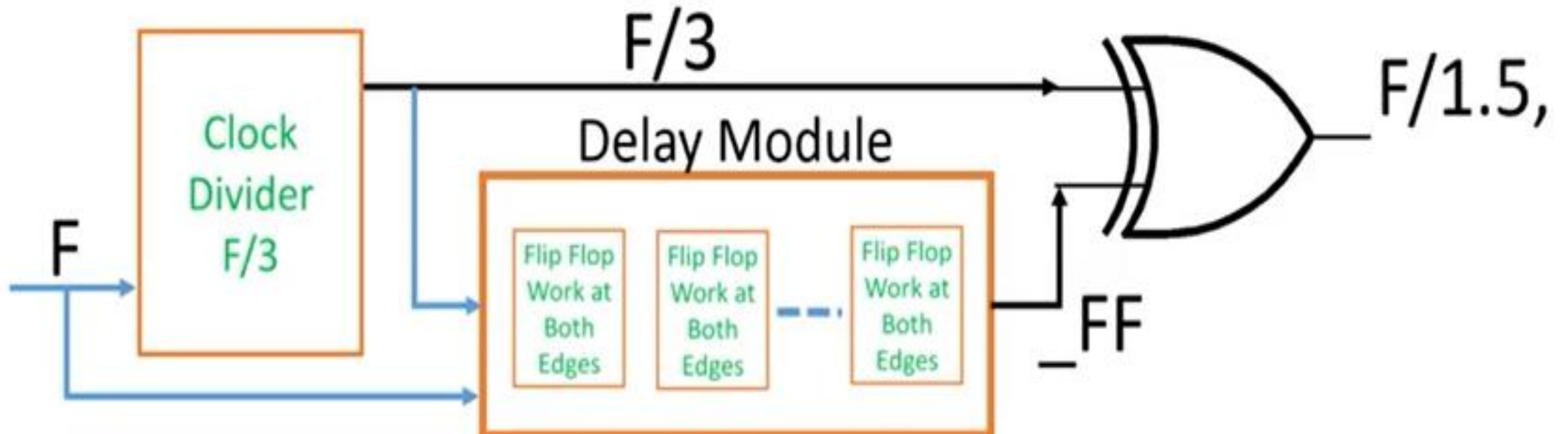

Frequency Divider for $f/1.5$

  

Frequency Divider for $f/1.5$

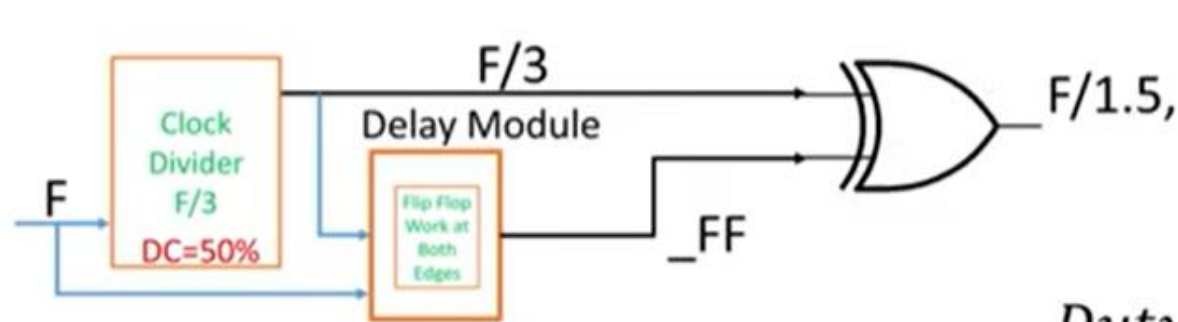 


$$\text{Duty Cycle} = \frac{T_{on}}{T_{on} + T_{off}}$$

$$\text{Duty Cycle} = \frac{T_{in}/2}{T_{in}/2 + T_{in}} = \frac{1}{3} \text{ or } 33.3\%$$



Conclusion for implementation of f/n divider

- Three building blocks are used to implement Frequency divider by a fractional number: Clock frequency divider by integer number, Delay Module and XOR gate.
- Multiply n by 2 and get the frequency ($f/2n$) to be generated by integer clock frequency divider. It is easy to generate $f/2n$ as $2n$ is integer number.
- Depending upon the duty cycle, decide number of flip flops to be added in the delay module.

Frequency Divider for $F/2.5$

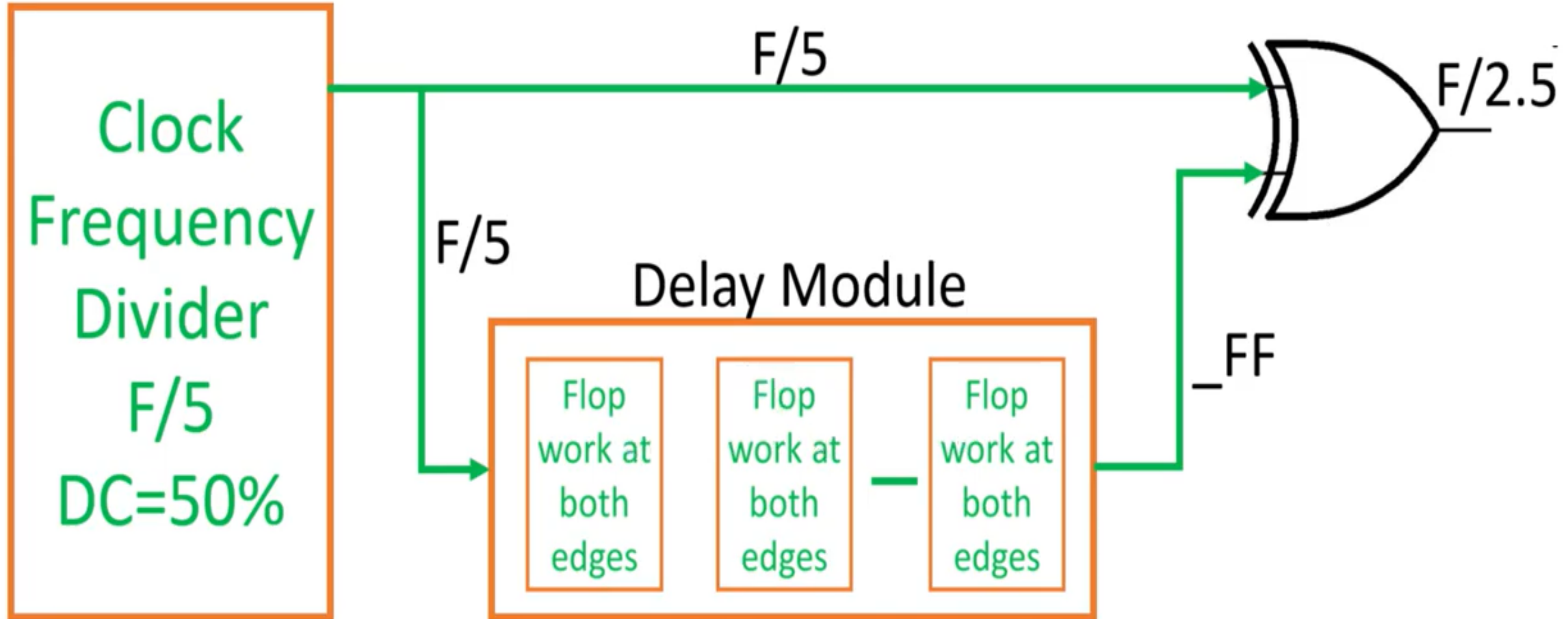



Frequency Divider for F/2.5

  

$$\text{Duty Cycle} = \frac{T_{on}}{T_{on} + T_{off}}$$

$$\text{Duty Cycle} = \frac{1}{5} \text{ or } 20\%$$



Frequency Divider for F/2.5

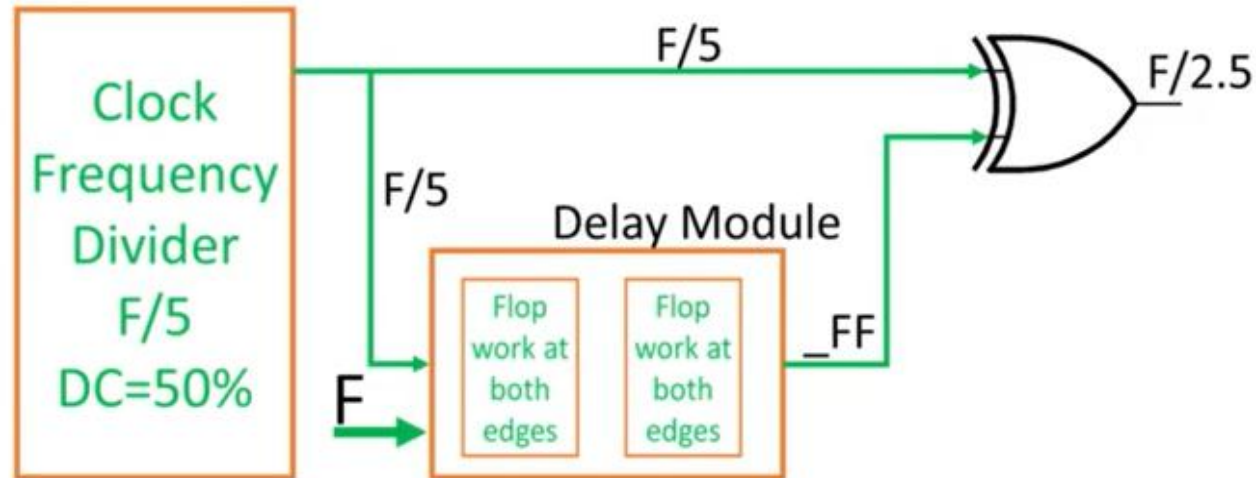 

$$\text{Duty Cycle} = \frac{T_{on}}{T_{on} + T_{off}}$$

$$\text{Duty Cycle} = \frac{2}{5} \text{ or } 40\%$$



Frequency Divider for $F/2.5$

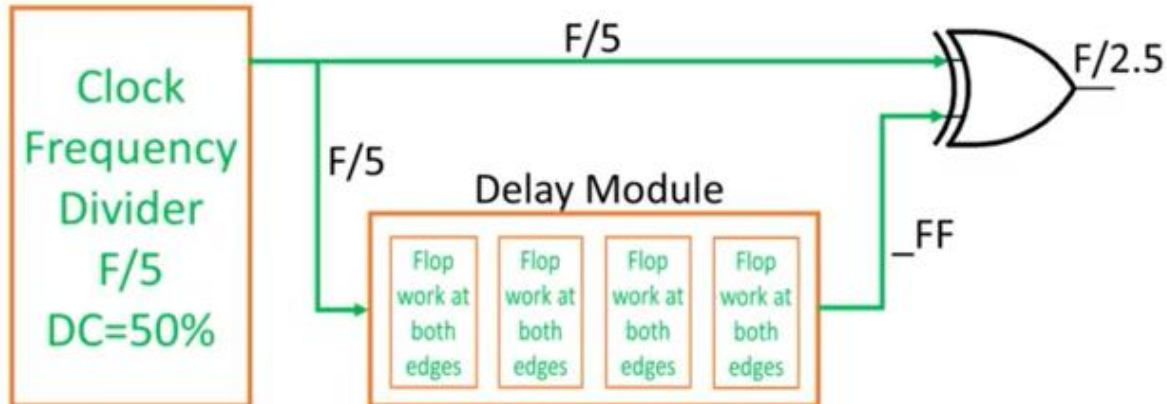 

$$\text{Duty Cycle} = \frac{T_{on}}{T_{on} + T_{off}}$$

$$\text{Duty Cycle} = \frac{4}{5} \text{ or } 80\%$$

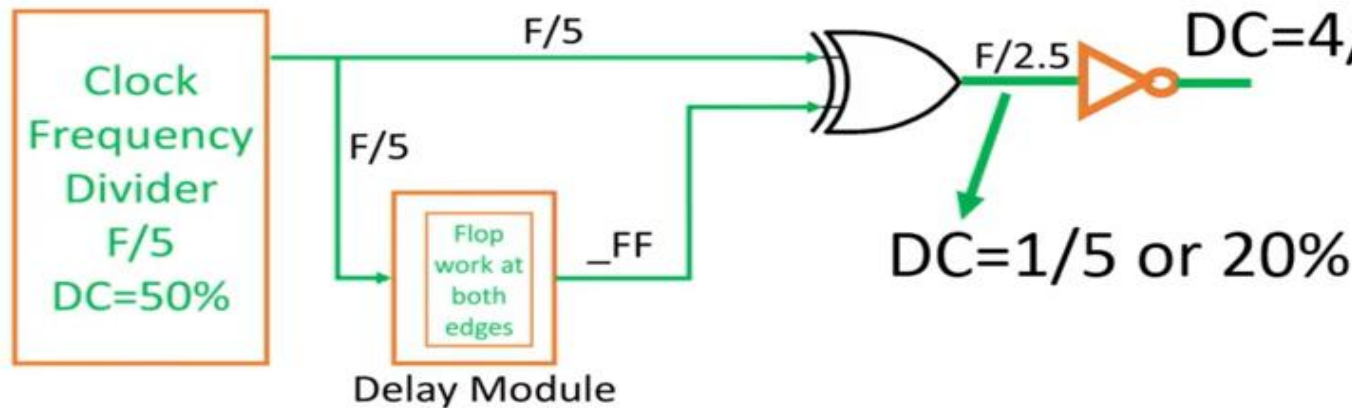 Hardware optimization for $F/2.5$, DC = $4/5$ or 80%



$$\text{Duty Cycle} = \frac{T_{on}}{T_{on} + T_{off}}$$

$$\text{Duty Cycle} = \frac{1}{5} \text{ or } 20\%$$

Conclusion for implementation of f/n divider

- Four building blocks are used to implement Frequency divider by a fractional number: Clock frequency divider by integer number, Delay Module, XOR gate, XNOR gate.
- Multiply n by 2 and get the frequency ($f/2n$) to be generated by integer clock frequency divider. It is easy to generate $f/2n$ as $2n$ is integer number.
- Depending upon the duty cycle, decide number of flip flops to be added in the delay module.
- Apply hardware optimization technique to reduce number of flip flops inside the delay module.